

How to make



- 1) Lock-in Amplifier
- 2) Current Source



By Sultan Abdul Wadood

# Introduction

- Used to recover a small signal buried in a large noise
- Essentially a band-pass filter with very narrow bandwidth and very low attenuation
- Accomplishes this by phase sensitive detection, as conventional filtering is not helpful

# Phase Sensitive Detection

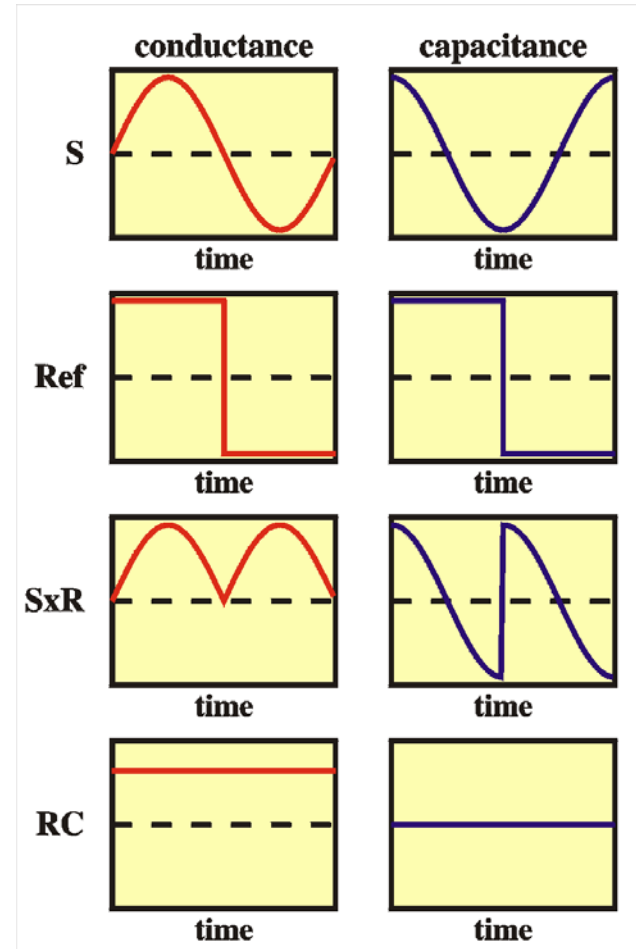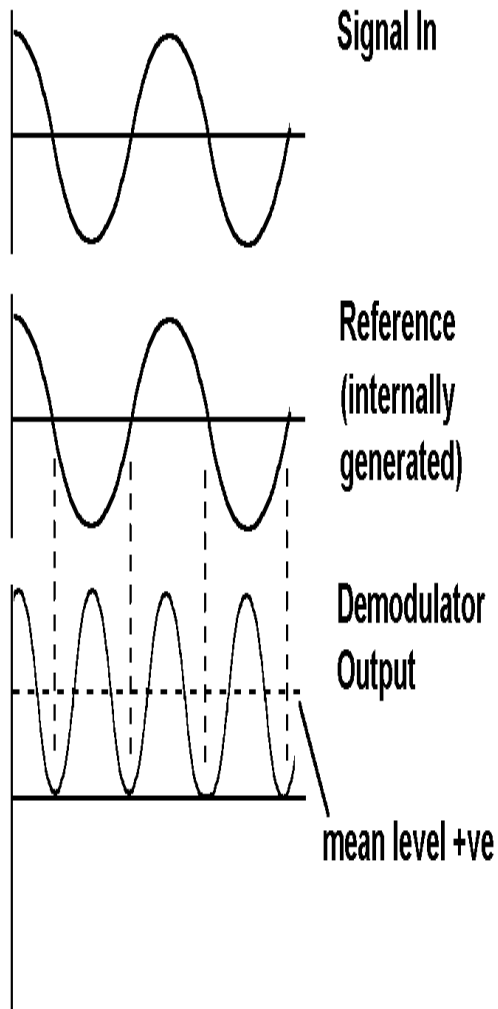

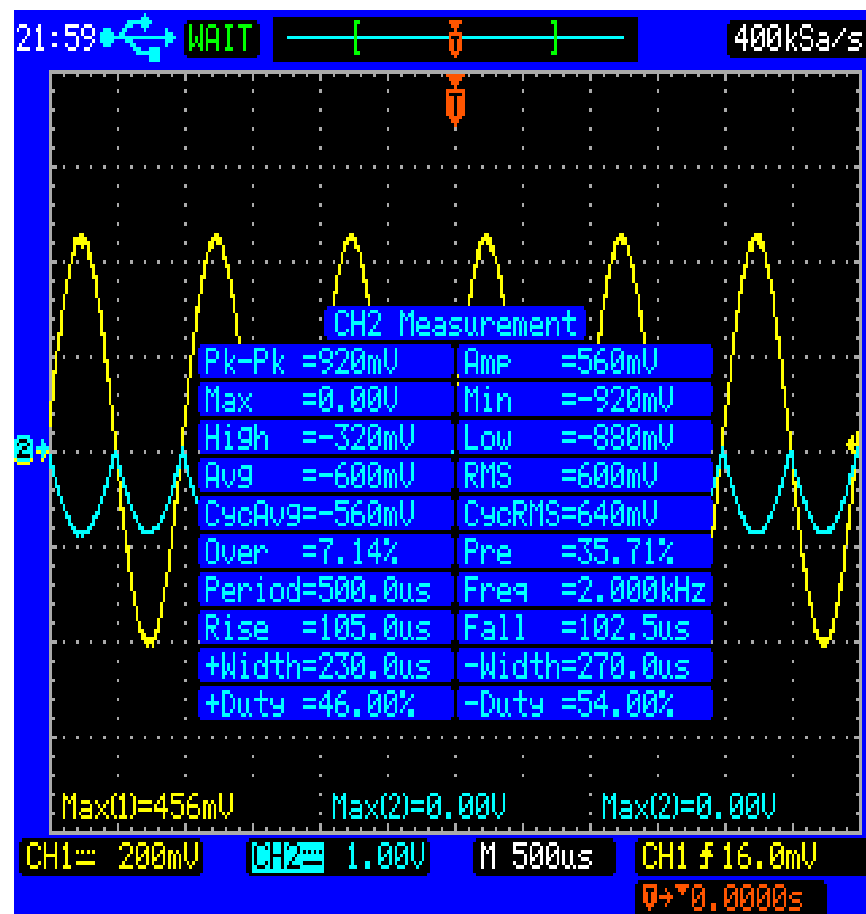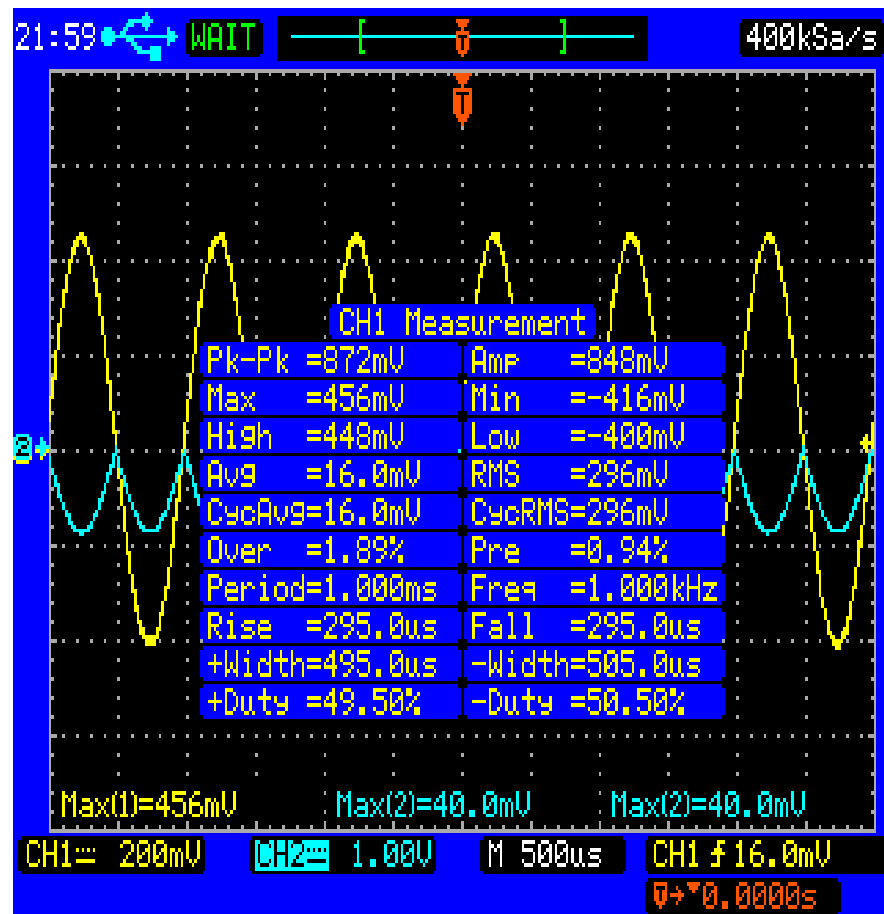

- Mixer/Multiplier
- Product of two sinusoids( $f_1$  and  $f_2$ ) is a signal containing two parts:
  1. Sum of frequencies
  2. Differences of frequencies

The mixer operates by multiplying the two signals together so, the output  $V_o$  will be,

$$V_o = A \sin(\omega t) B \sin(\Omega t + \phi) \quad (3)$$

$$= \frac{AB}{2} (\cos((\omega - \Omega)t + \phi) - \cos((\omega + \Omega)t + \phi)), \quad (4)$$

showing that the mixer output comprises two AC signals, one at the difference frequency  $(\omega - \Omega)$  and other at the sum frequency  $(\omega + \Omega)$ . If reference frequency is equal to the frequency of input signal i.e.  $\omega = \Omega$ , a sinusoidal output is obtained with some DC offset Figure (5).

$$V_o = \frac{AB}{2} (\cos(\phi) - \cos(2\Omega t + \phi)). \quad (5)$$

So, the output  $V_o$  is proportional to the magnitude of input signal A, the cosine of angle between input and reference and it is modulated at twice the reference frequency.

- Our Mixer will multiply the incoming signal with a square wave, which will create some problems, more on this later.

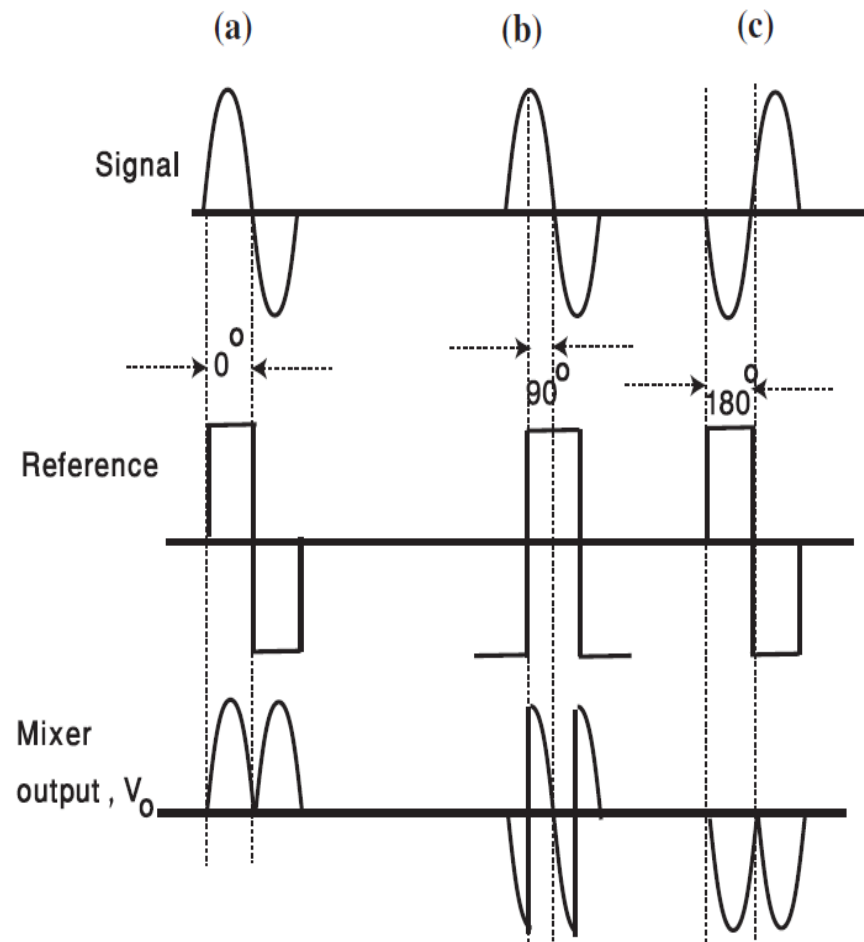



Figure 5: The output  $V_o$  is determined by multiplying the signal and the reference wave.



# Home Brew Lock-in Amplifier

- Four Parts:
  1. Input Amplifier (AD620)
  2. Mixer (AD630)
  3. Low Pass Filter (Single Pole)
  4. Output Amplifier (OP 27)


# Lock-In Amplifier

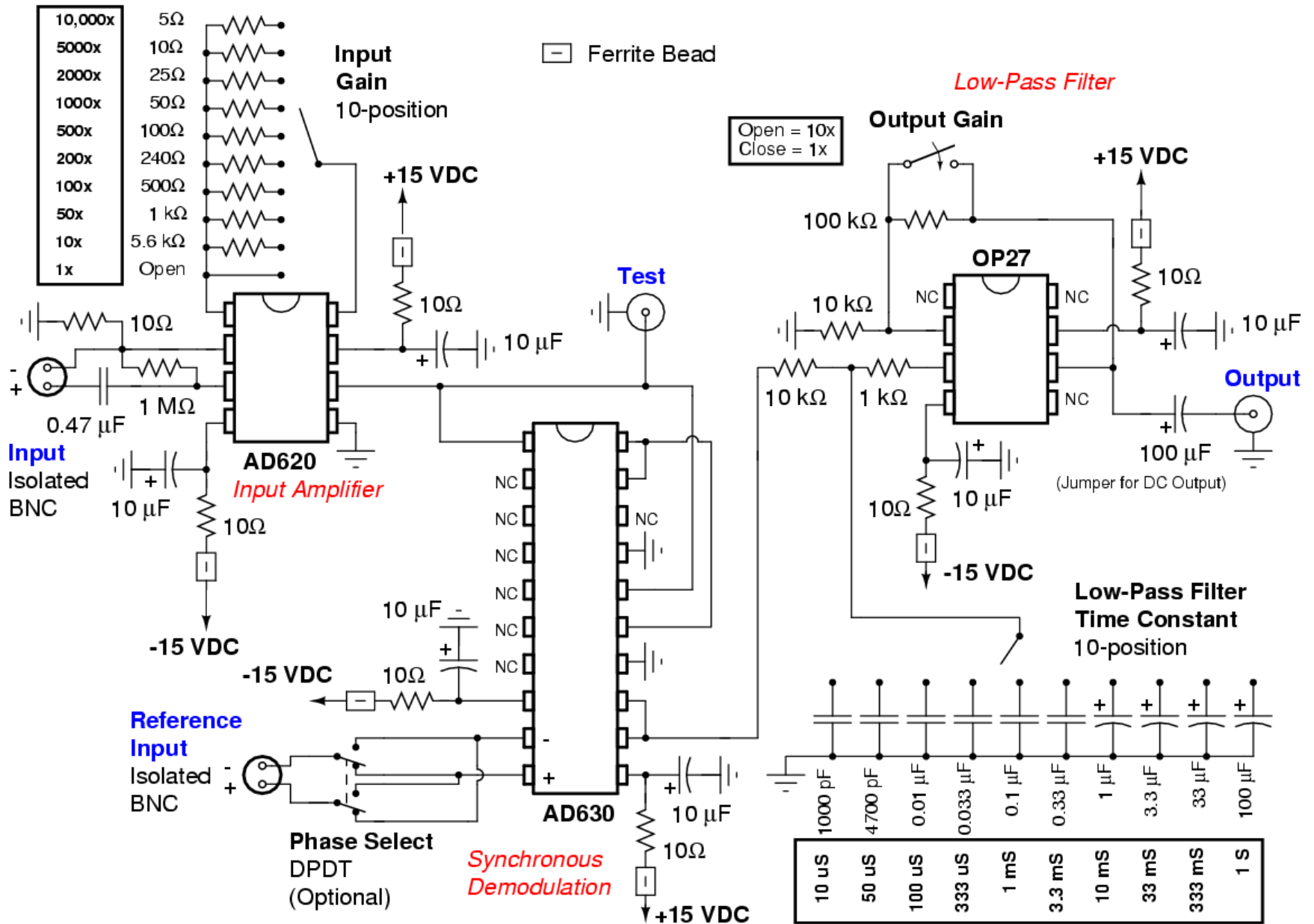

# Noise and Other Terms


- Many types of noise but we have restricted ourselves to White Noise and  $1/f$  noise.
- Inherent Worst noise figure of  $75.83\mu\text{V}$ .
- Dynamic Reserve= Ratio of Overload level of noise to full scale input signal
- SNR:Signal to Noise Ratio
- 1MHz unity gain bandwidth of AD620

- Measurement of resistance of a wire

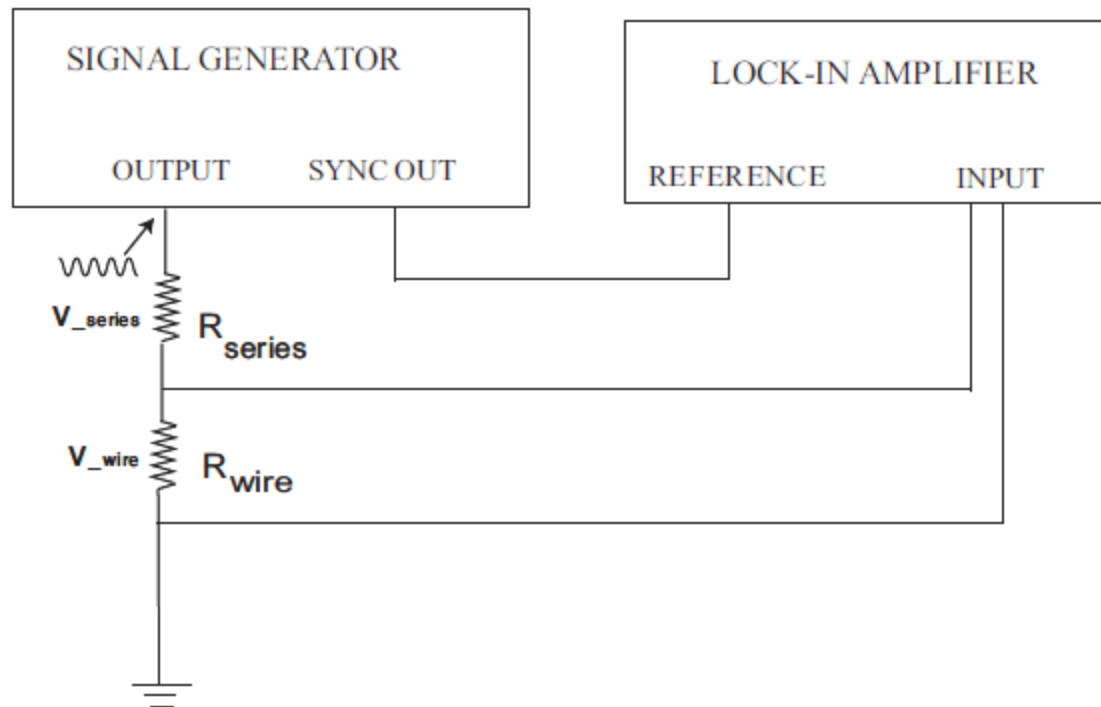

Note new toolbar buttons: [data brushing](#) & [linked plots](#)   [Play video](#)

×

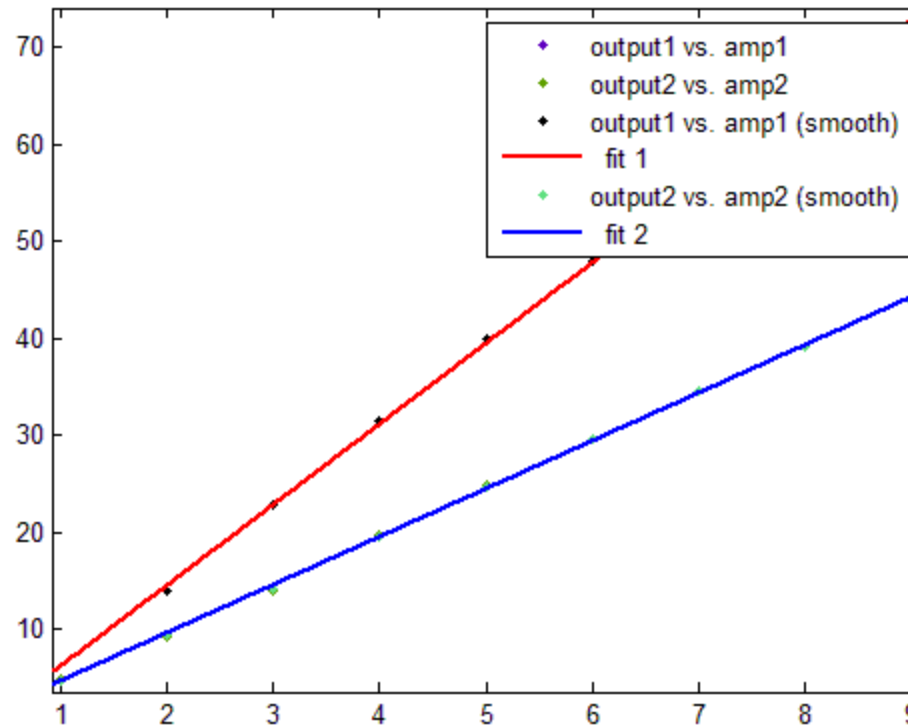

Y-axis: Voltage drop across wire in mV.

X-axis: Amplitude of Source

- Commercial:22.3mOhm
- Homebrew:14m Ohm
- Erroneous Results.

# Malus's Law Verification

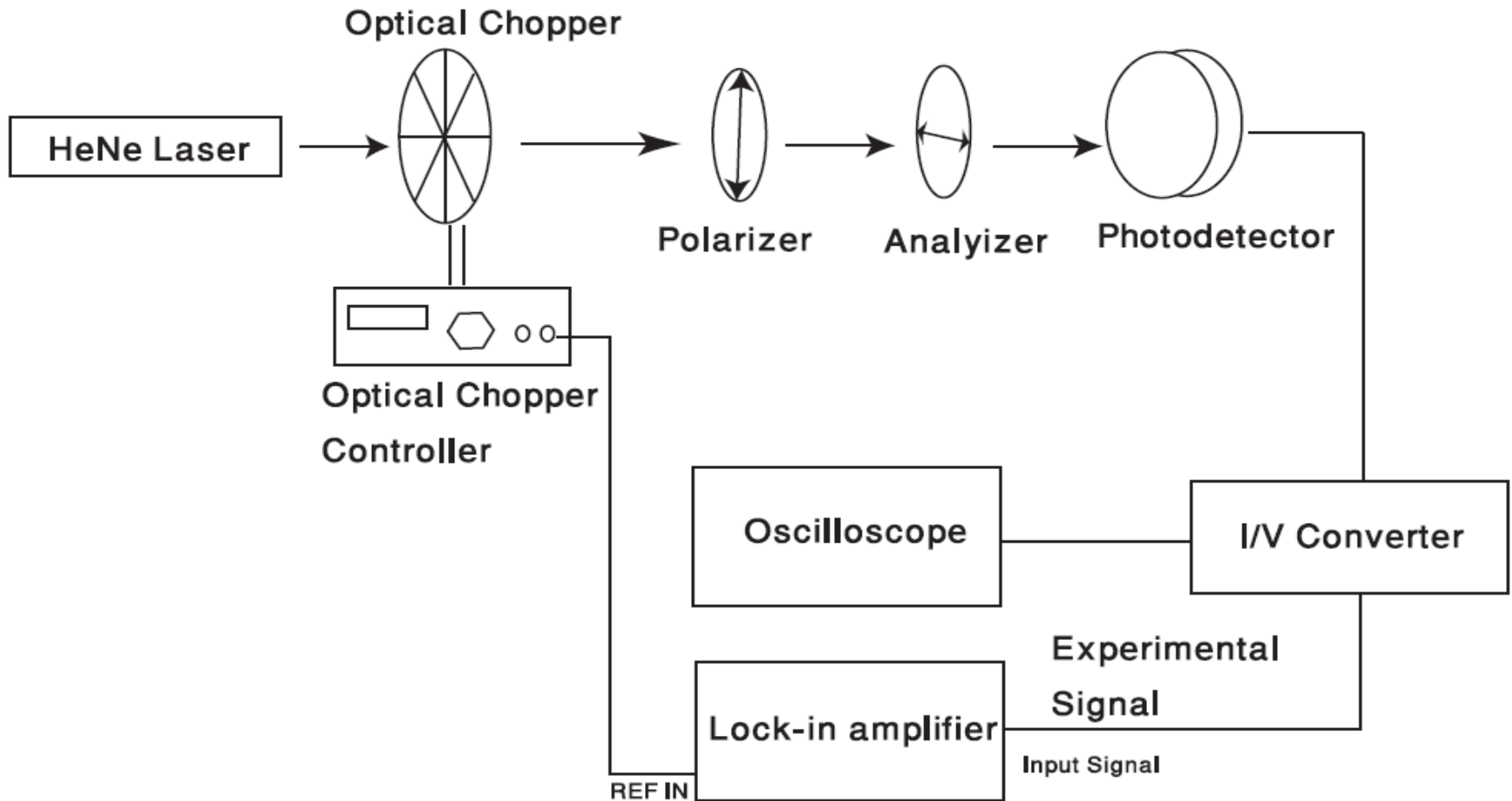


Figure 6: Weak Signal Measurement.

- Main Test was Malus's law which states :
- **According to malus, when completely plane polarized light is incident on the analyzer, the intensity  $I$  of the light transmitted by the analyzer is directly proportional to the square of the cosine of angle between the transmission axes of the analyzer and the polarizer.i.e  $I \propto \cos^2\theta$**




# Results

- Large Deviation from the Commercial Lock-ins.
- Cursory measurements to be avoided.
- Further Testing required.
- Improvements like PLL, dual phase, phase shifter etc. can be made.

- This year, with some little tweaks, better results have been obtained.

# Verification of Malus's Law

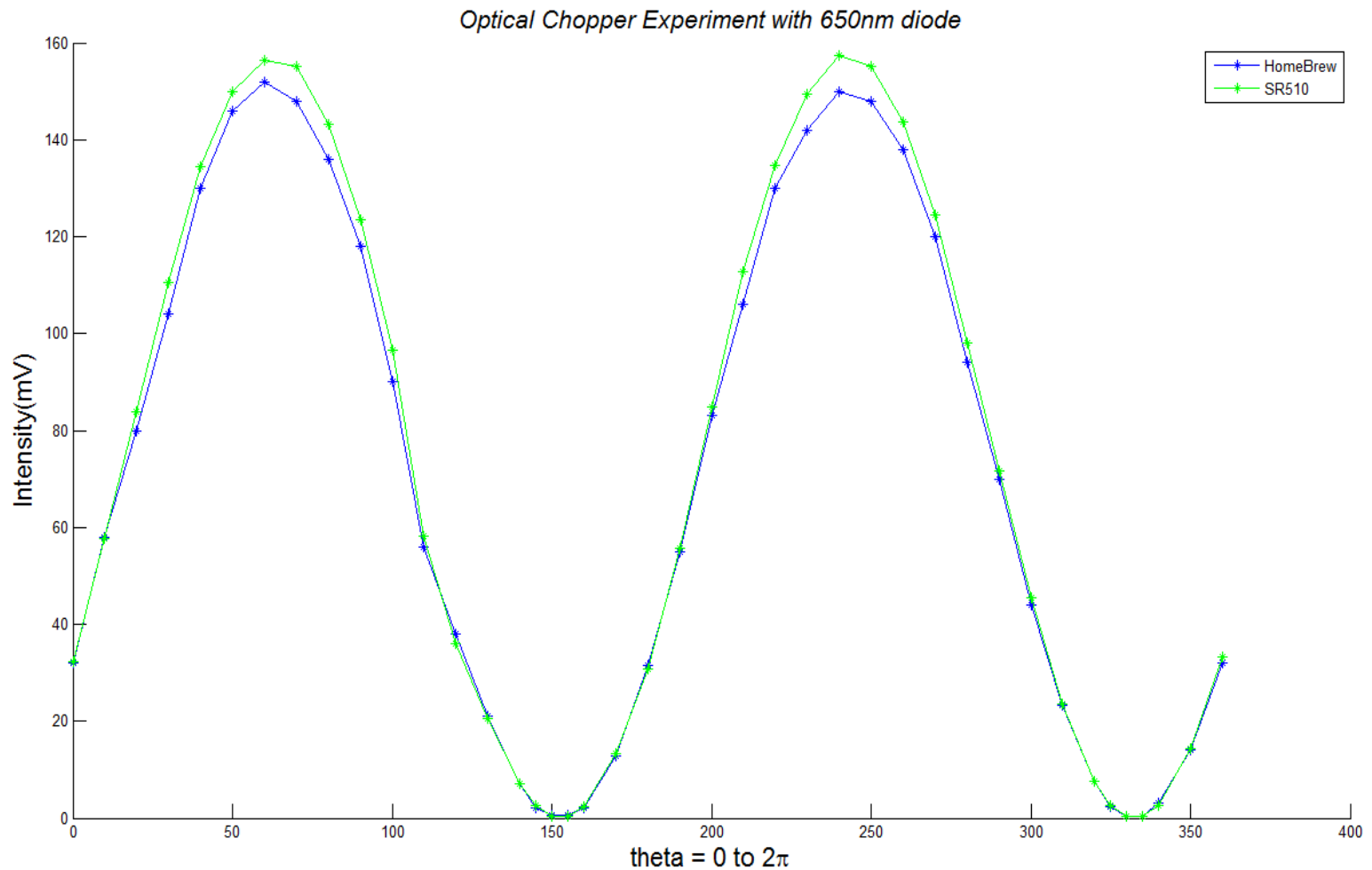


# Two Main Problems

- Line Hum reduction
- Proper reading of photodiode output through trans-impedance Amplifier

# Week 1

- Observed a 100mV amplitude 50Hz wave at input even though the circuit was powered off


# Hum

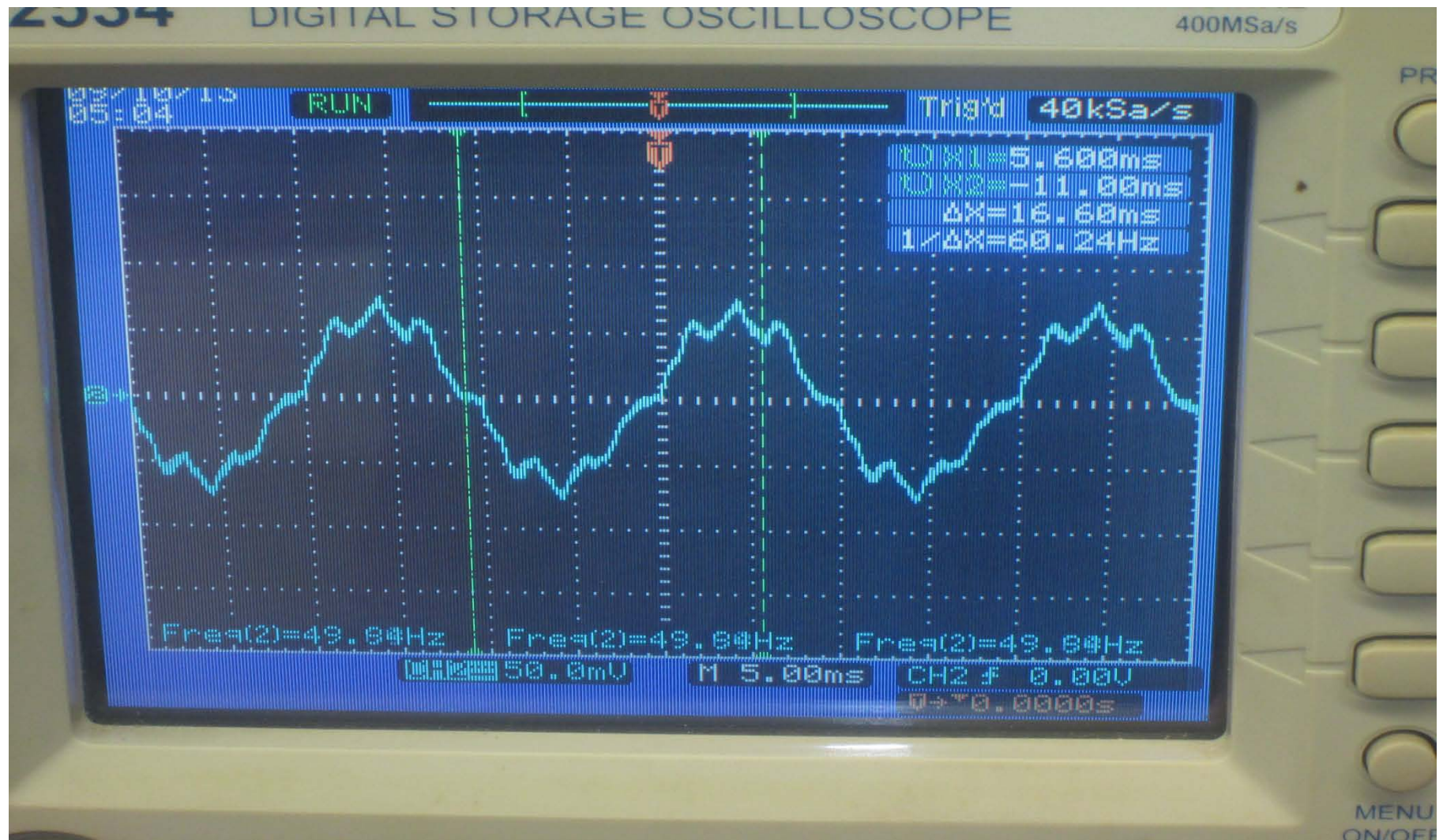

- Natural Option to deal with it was a notch filter
- But Notch are RLC filters, and inductors must be avoided in precision circuits.
- An inductor-less notch is a 'twin-tee' notch.


Twin-T active notch filter

$$f = \frac{1}{2 \pi R C}$$

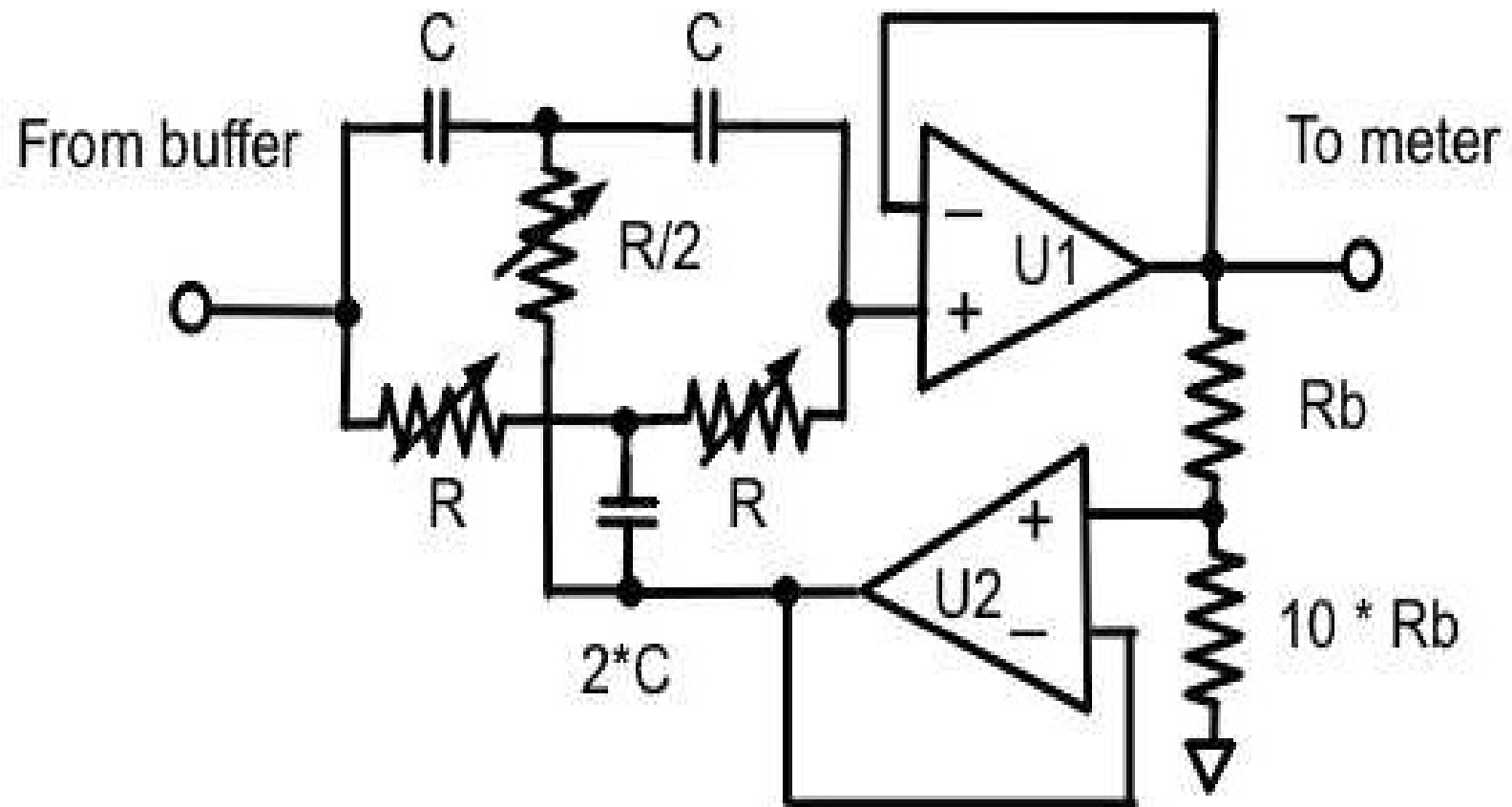



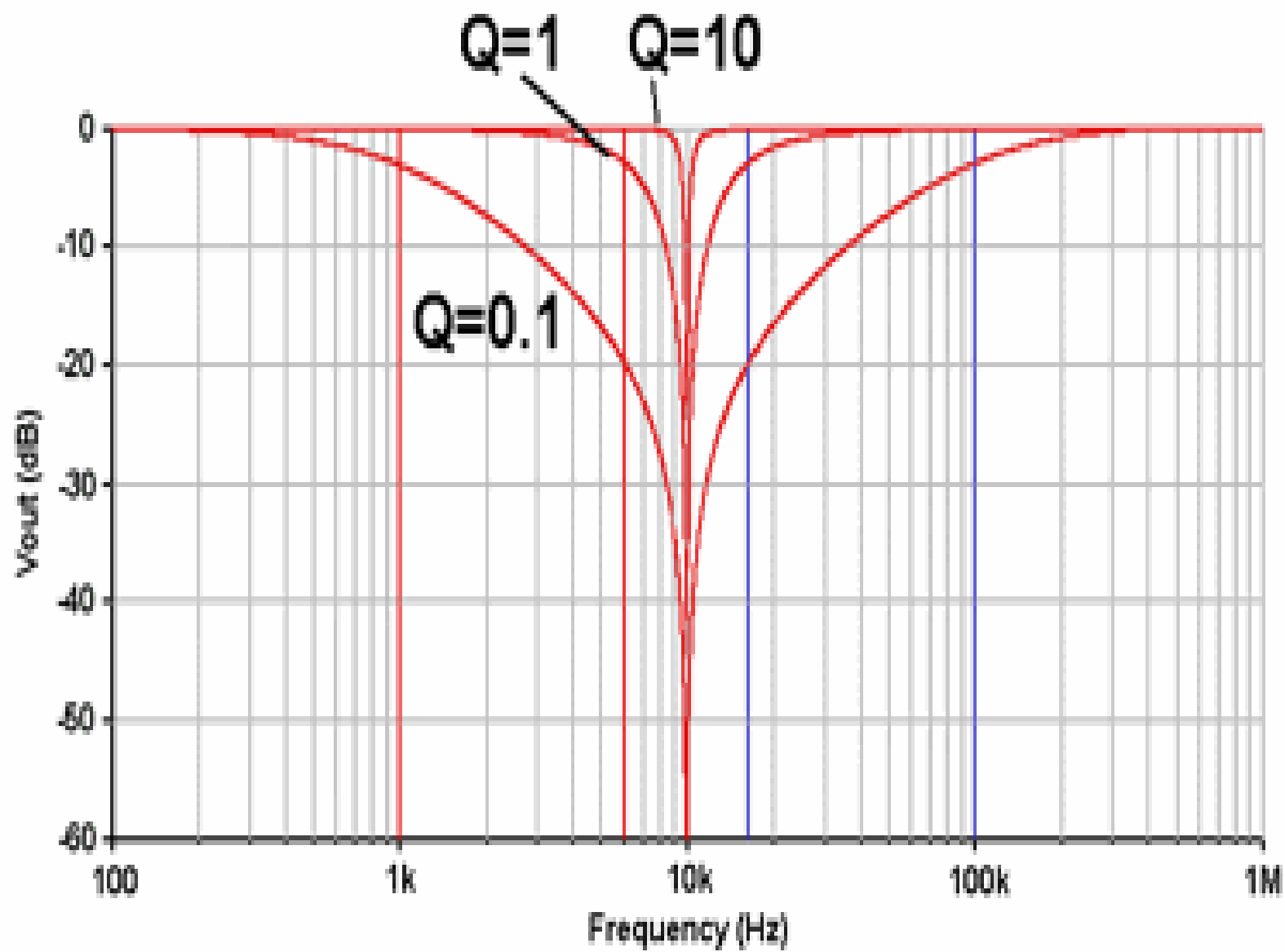- Recursive Problem: We need a high Q 'Twin-T' notch to remove hum for building a lock-in amplifier, which is itself a very-high-Q notch.
- Line-in option in SR510 for hum removal.
- Low Q notches were made.(Max. depth of 28.8dB) and using AD620 as op-amp instead of UA741 for high precision.
- Bandwidth was very high(of the order of 100kHz)
- $Q = \omega / B.W$



- The AD630 data sheet mentions recovering 50 $\mu$ V of signal from 100dB of noise(5V).
- So I tried this circuit:

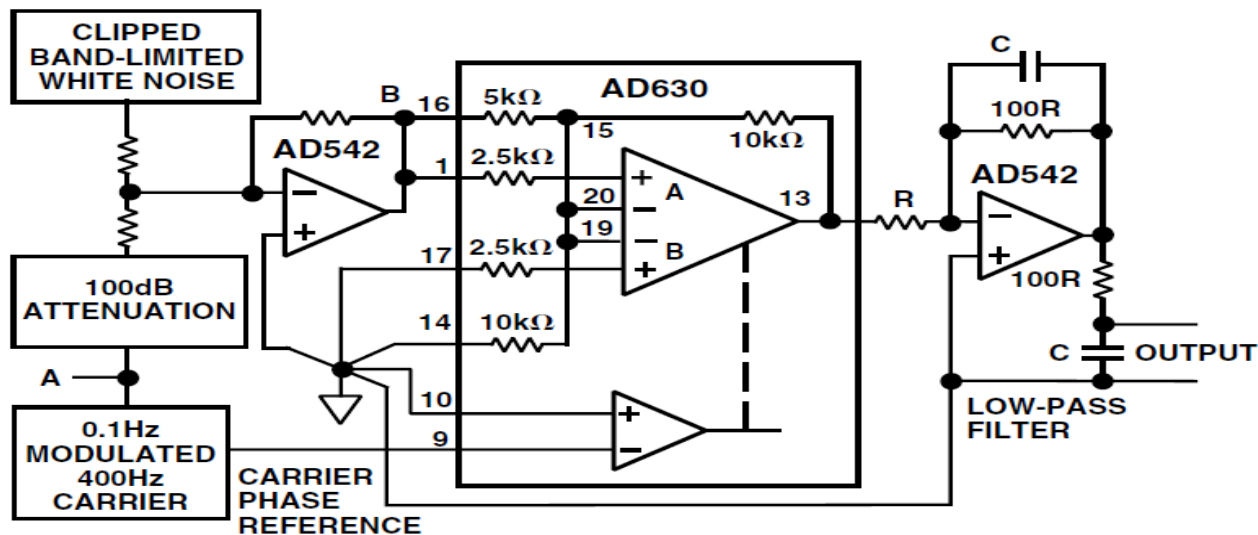


Figure 14. Lock-In Amplifier

- Maybe the AD630 would take care of hum itself and I won't have to AC amplify the signal.
- But there was another problem with my measurement of photodiode output.
- I was also exploring the option of shielding.

# Week 2

- Stray thoughts on the reasons for wrong results of Optical Chopper experiments, overloading, non-linearity, PLL?
- Put the circuit in an Al-foil enclosed box. Hum was reduced but still observed funny effects. The Al-foil was not grounded.


# Al Foil



# An Eid spent in the Car

- Jana, Eid par aana, phir ghar jana, phir wapis Lahore Aana.
- Talked to some experts, they told me to ground the foil.

# Hum with Al shielding

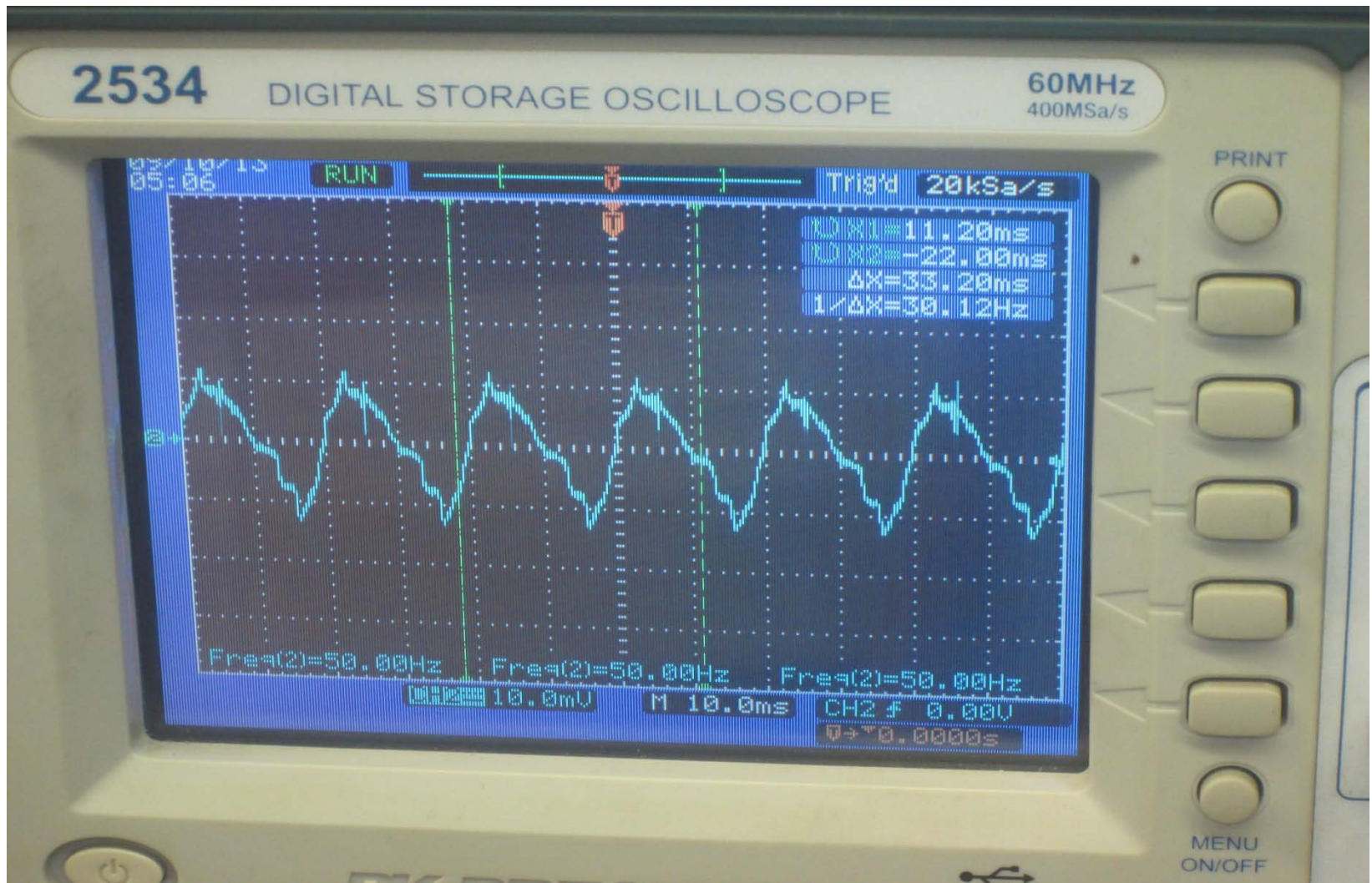



Ground the Foil at various Points to ensure uniform grounding



# Week 3

- Read more upon noise removal and proper grounding.
- Rarely Asked Questions on Bread boarding.
- Basic Principle of Noise Reduction:
- COPPER IS NOT A SUPERCONDUCTOR

# CAPACITANCE

Wherever two conductors are separated by a dielectric (including air or a vacuum) there is capacitance.

For a parallel plate capacitor  $C = \frac{.0885 E_r A}{d} \text{ pF}$

where A is the plate area in sq.cm


d is the plate separation in cm

&  $E_r$  is the dielectric constant

Epoxy PCB material is often 1.5 mm thick and  $E_r = 4.7$



Capacity is therefore approximately 2.8 pf/sq.cm

# CAPACITOR LEADS MUST BE SHORT

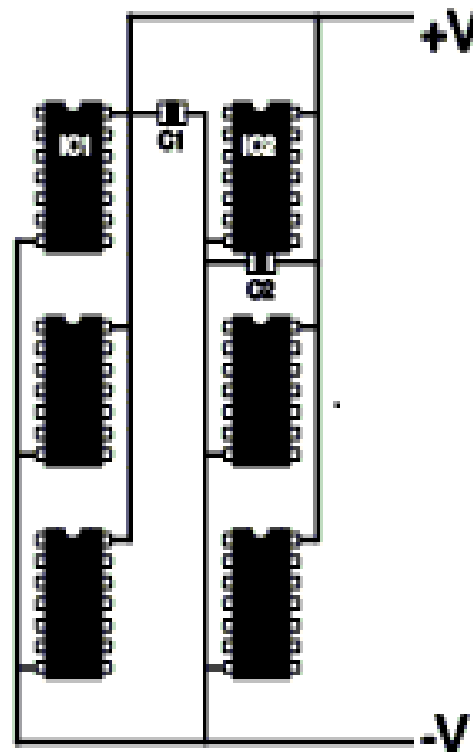

Although the leads of C1 are short the HF decoupling path of IC1 is far too long.  
The decoupling path of IC2 is ideal.

# INDUCTANCE

 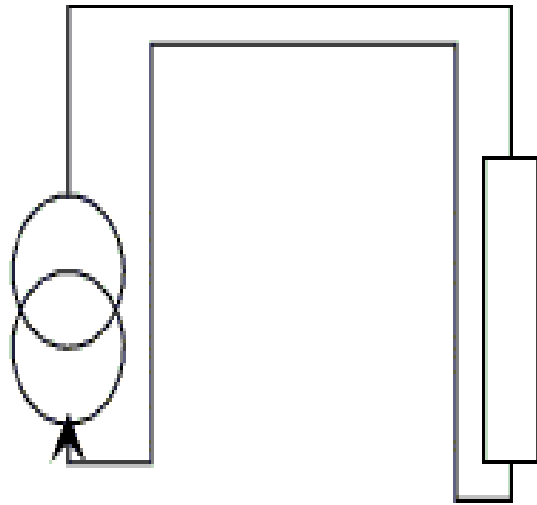

Inductance is reduced by reducing loop area -  
mutual inductance is reduced by reducing loop area  
and increasing separation.

Since the magnetic fields around coils are dipole fields they attenuate with the *cube* of the distance - so increasing separation is a very effective way of reducing mutual inductance.

# OBEY THE LAW

Unexpected behaviour of analog circuitry is almost always due to the designer overlooking one of the basic laws of electronics.

Remember and obey Ohm, Faraday, Lenz, Maxwell, Kirchoff  
and **MURPHY.**

- Grounding the foil reduced Hum to 2-3mV from 50mV.
- Twisting cables are better than straight ones.
- Differential Input: Required or not.

# Weekend


- Met Prof. Shameem: Says that life is a tragedy, we will never know the truth and will die hunting for it.(So is the case of Noise with precision circuits).



# Week 4

- Studied AD630 in more detail, resistors reducing input bias current, frequency compensation.
- Saw other works using Ad630 as a lock-in.
- Realised all of them were working on mV scale, not uV.
- Accurate voltage readings till 1mV with simple voltage dividers.
- In one [project](#), PSPICE simulation could provide maximum SNR of 45dB, instead of the data sheet's 100dB.
- Zeroing the phase of SR510.


<b>Vin</b>	<b>Vnoise</b>	<b>Sign/Noise</b>	<b>Gamp</b>	<b>Demod.</b>	<b>Simulazione:</b>
$V_{pp}$	$\frac{V_{eff}^2}{Hz} (1Khz)$	$\frac{S}{N} (dB)$	$20Log\left(1 + \left(\frac{R_2}{R_1}\right)\right)$		Red=Input 100 Hz Green=Out Demodulated
0.01V	$1.90 \frac{V_{eff}^2}{Hz} (1Khz)$	-45 dB	46 dB	No	

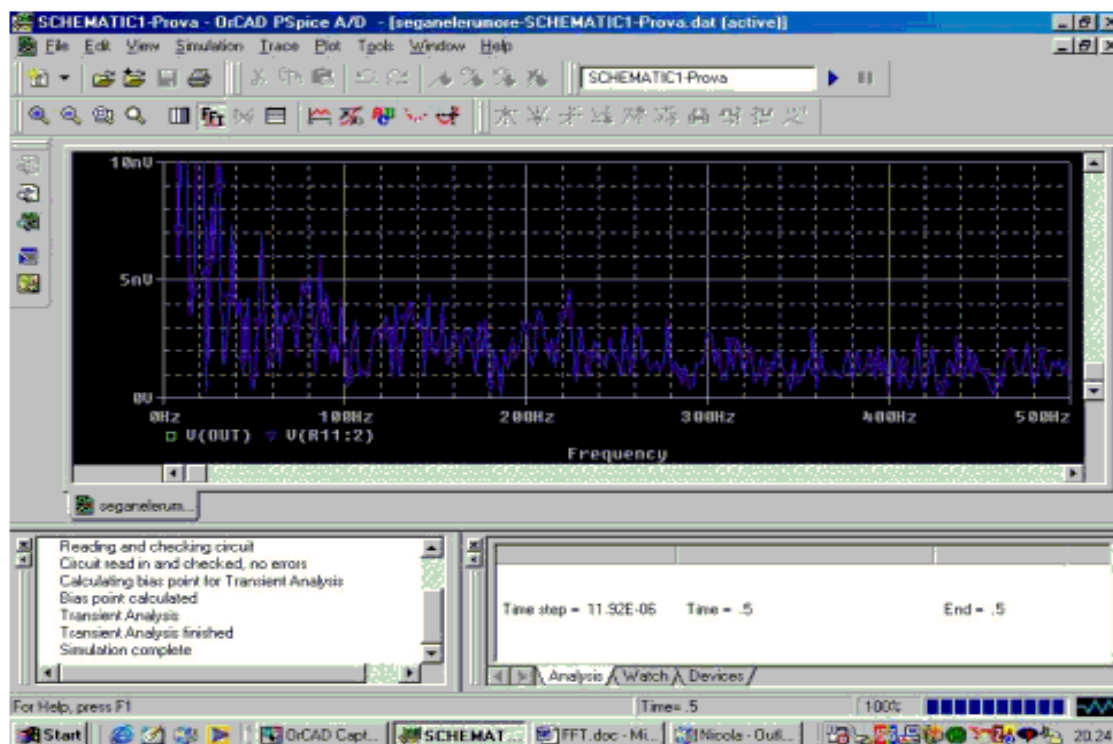


The Pspice© simulation given some important result, we can't confirm the Analog Device result obtained at 1 Khz but we could be satisfy for our  $-45 \text{ dB} \left( \frac{S}{N} (dB) \right)$  a 100 Hz.


# Week 5

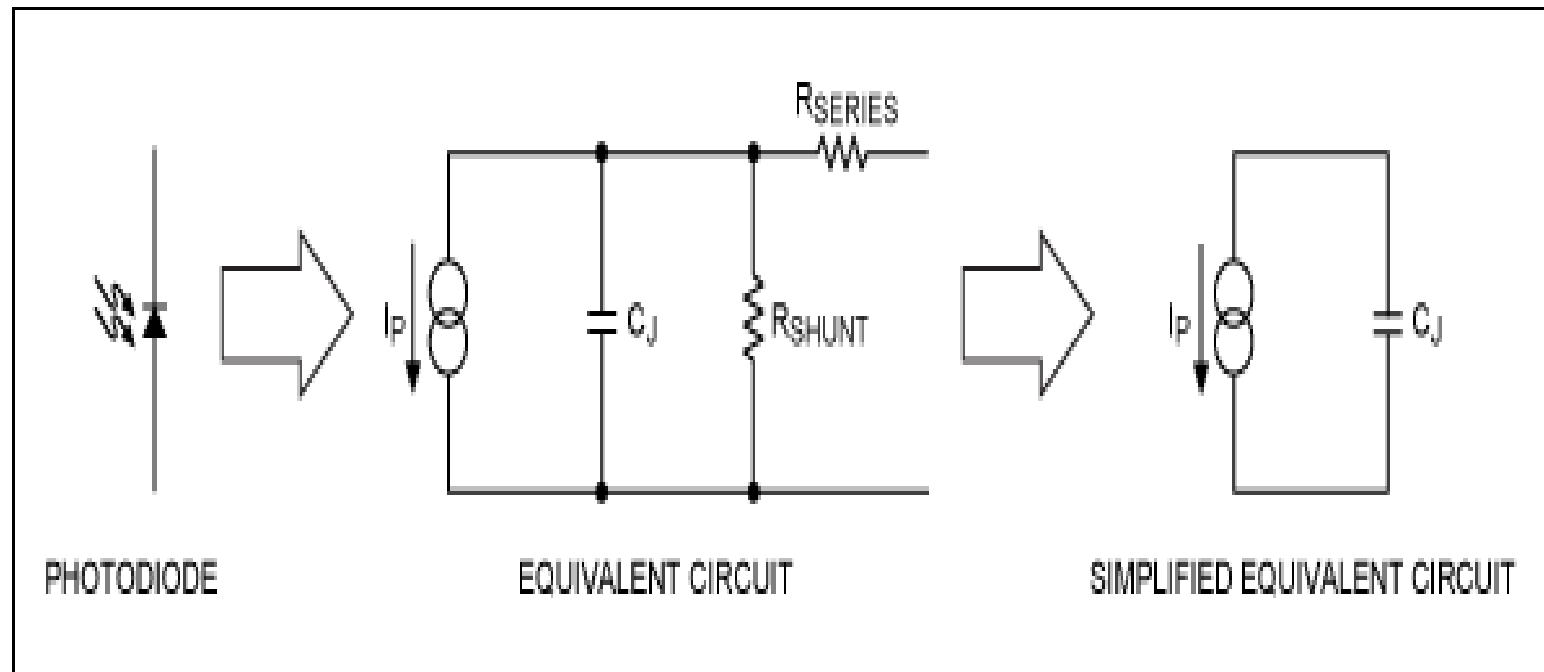- Trans-Impedance Amplifier
- Photo Diode Model:




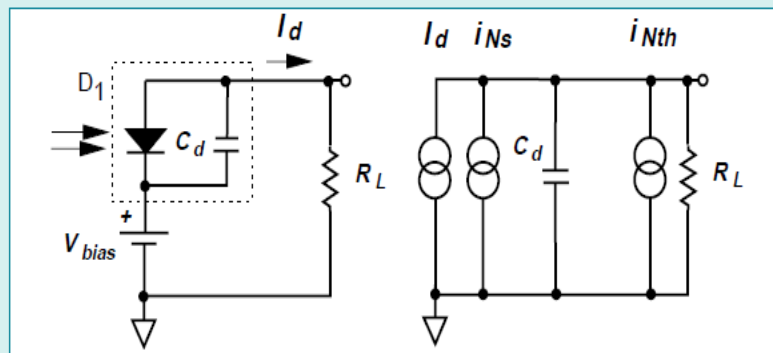


**Figure 1.** The world's simplest front end: a load resistor.

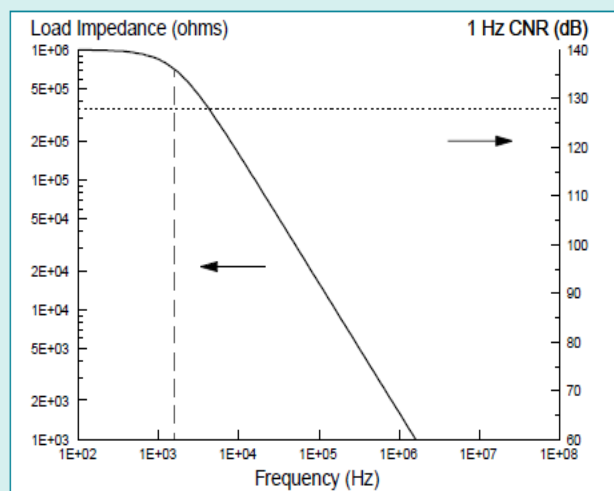

**Figure 2.** Photodiode/load resistor circuit: frequency response and 1 Hz SNR.

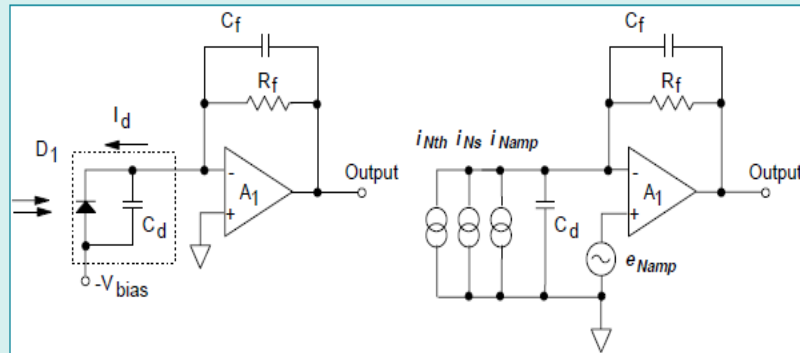


**Figure 3.** Transimpedance amplifier schematic and noise model.

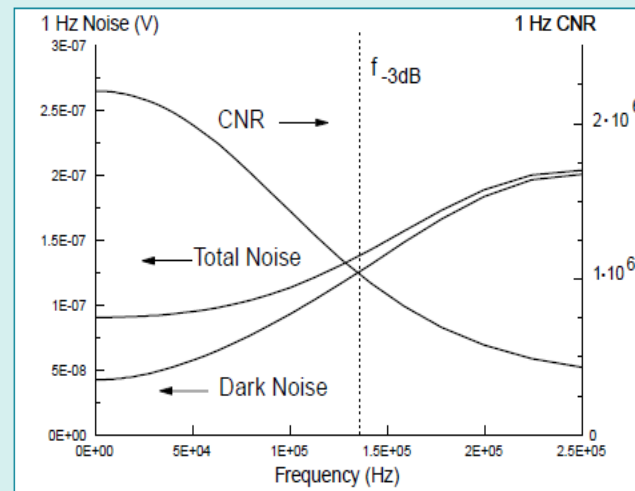


**Figure 4.** Noise performance of the transimpedance amplifier of Fig. 3, showing the dominance of  $e_{Namp}$  at high frequency.  $A_1$  is an LF356,  $R_f=100k\Omega$ ,  $C_f=0.5$  pF.

# Basic Trans-Impedance Amplifier


- Gain is equal to  $R_f$  (V/A or Ohm)

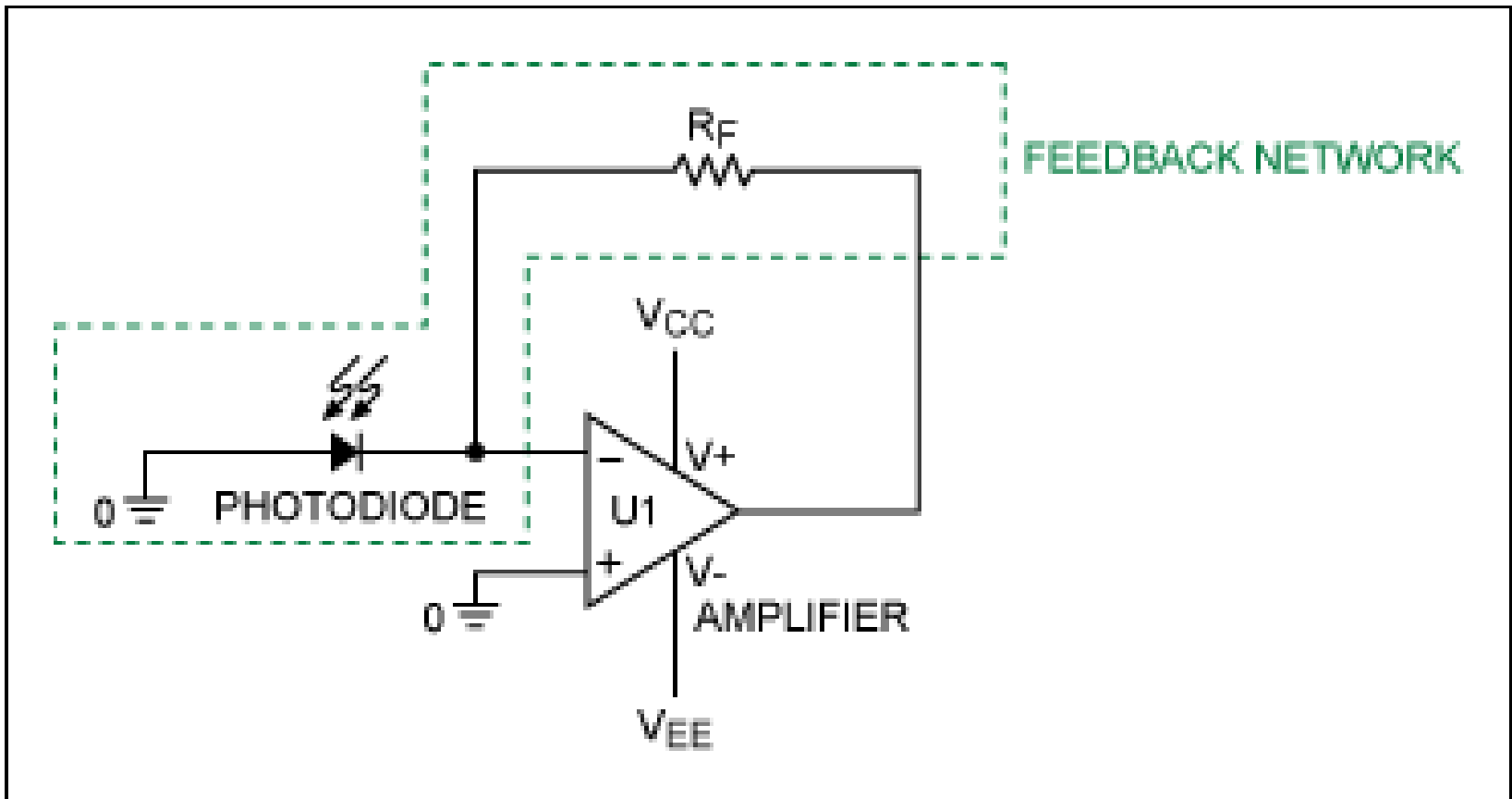


# Barkhausen stability criterion

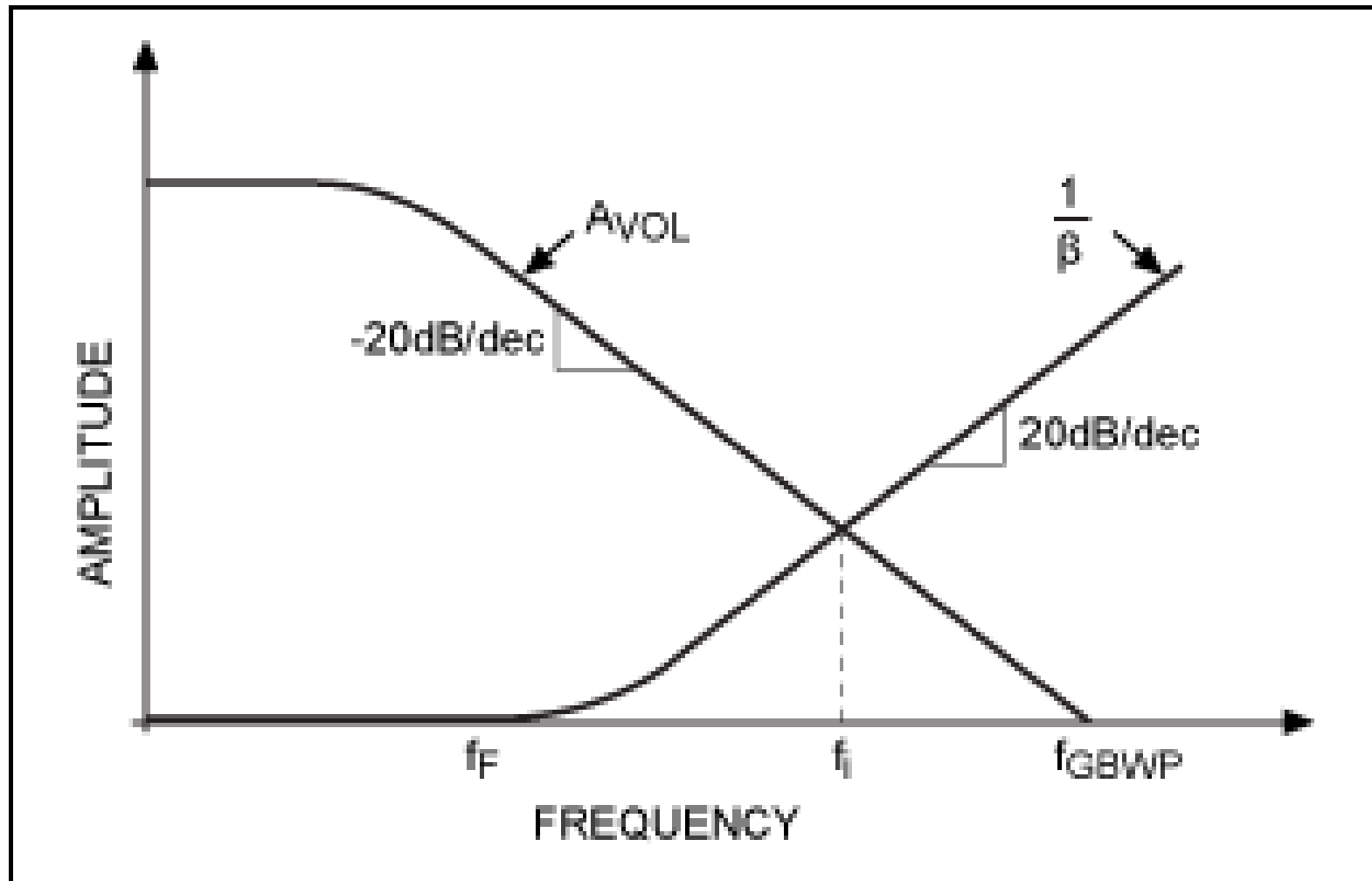

# Compensation Feedback Capacitor

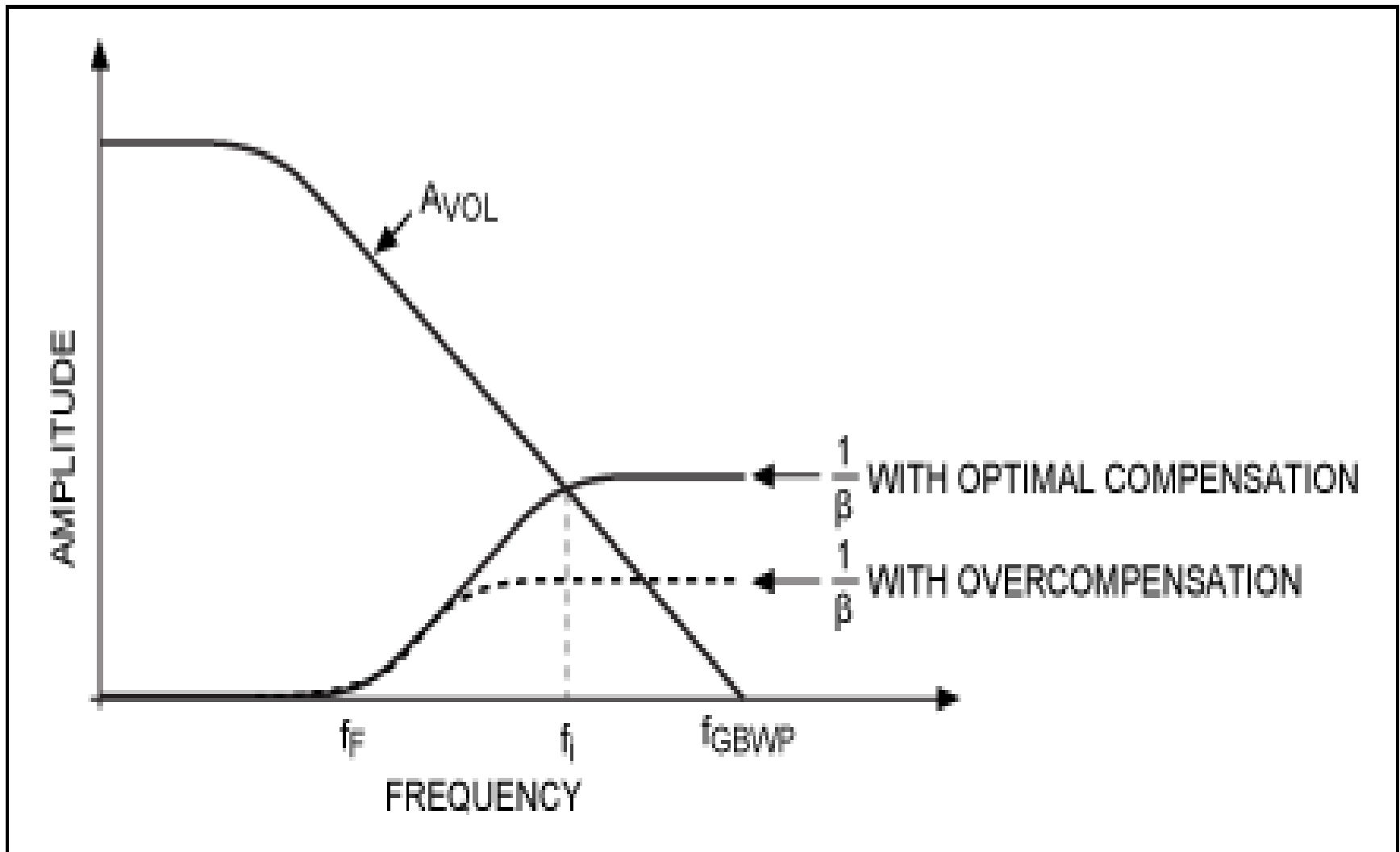

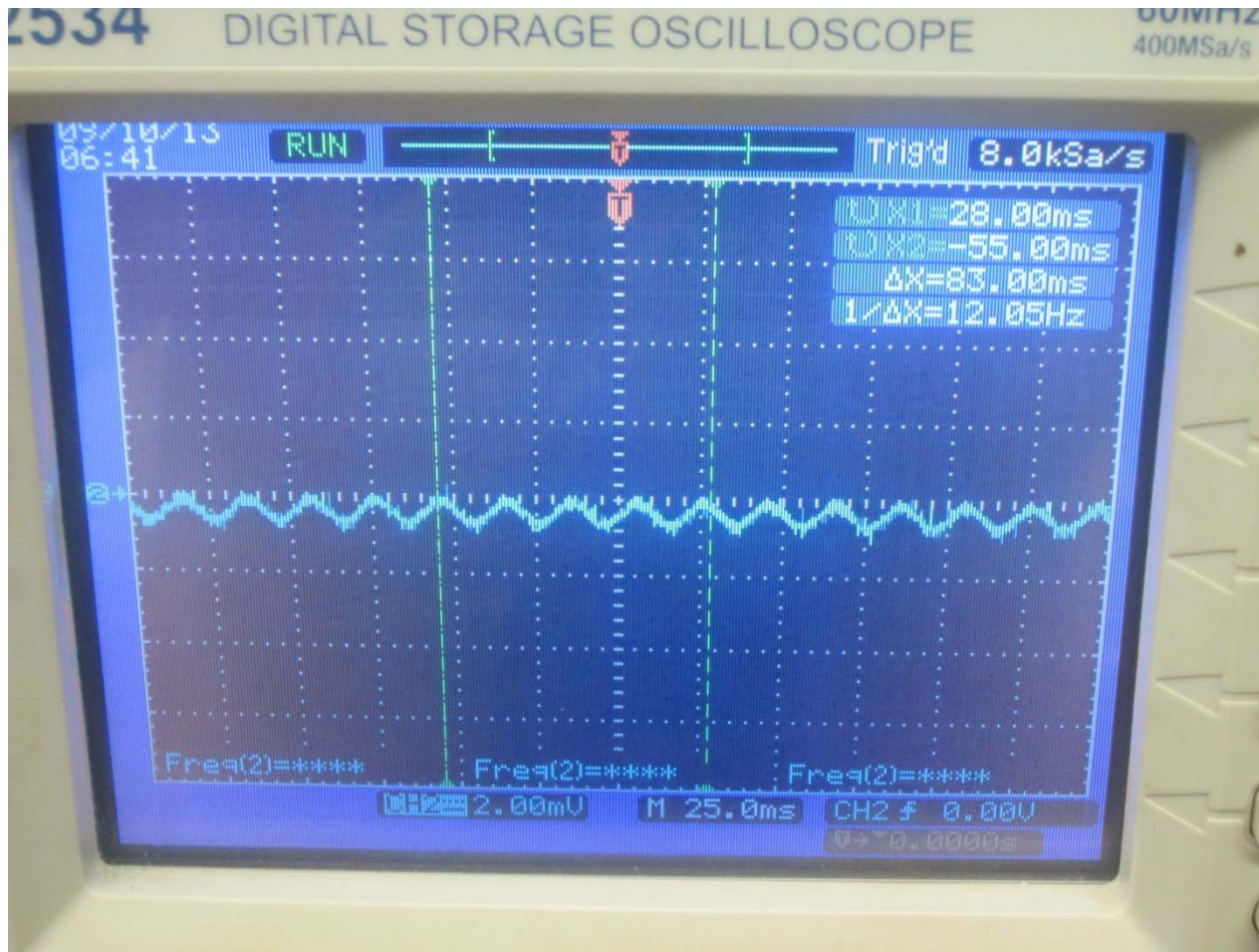
# Directly Connecting Photodiode output to Oscilloscope






# Ringling and Oscillation

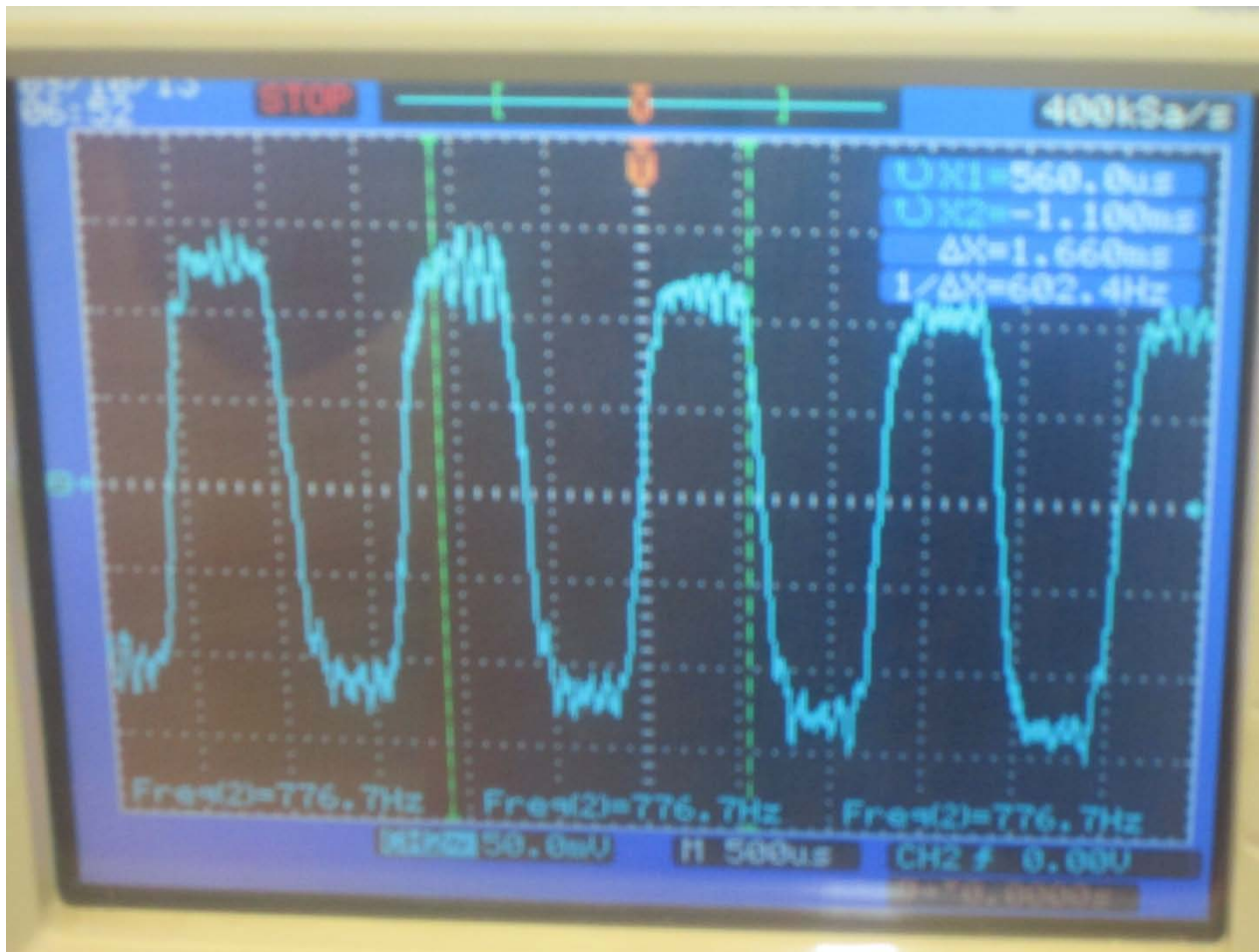


# After adding feedback capacitor

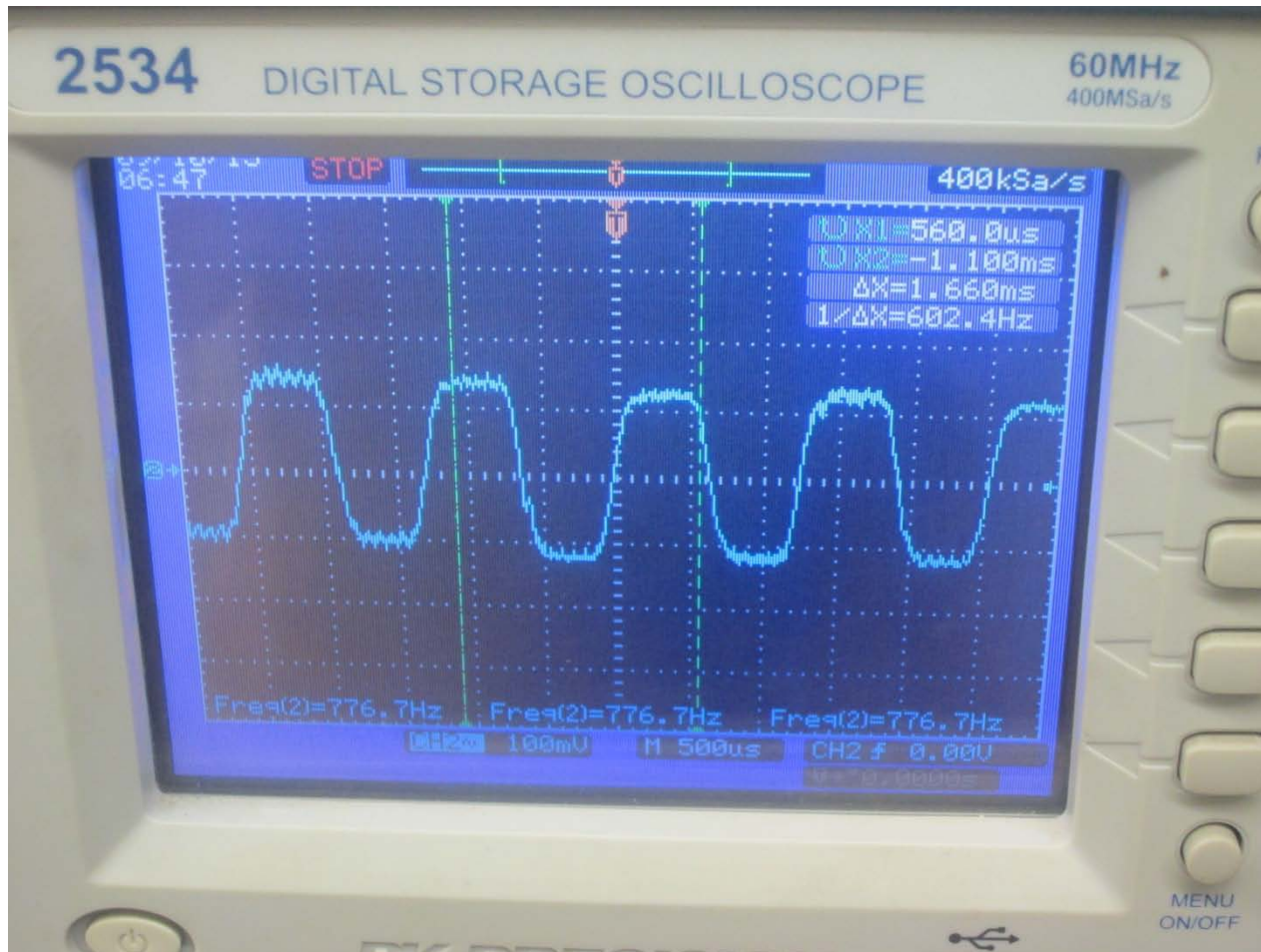

# Results


- The 4mW He-Ne Laser was used first. The results were a bit eerie owing to the unstable output of the Laser.
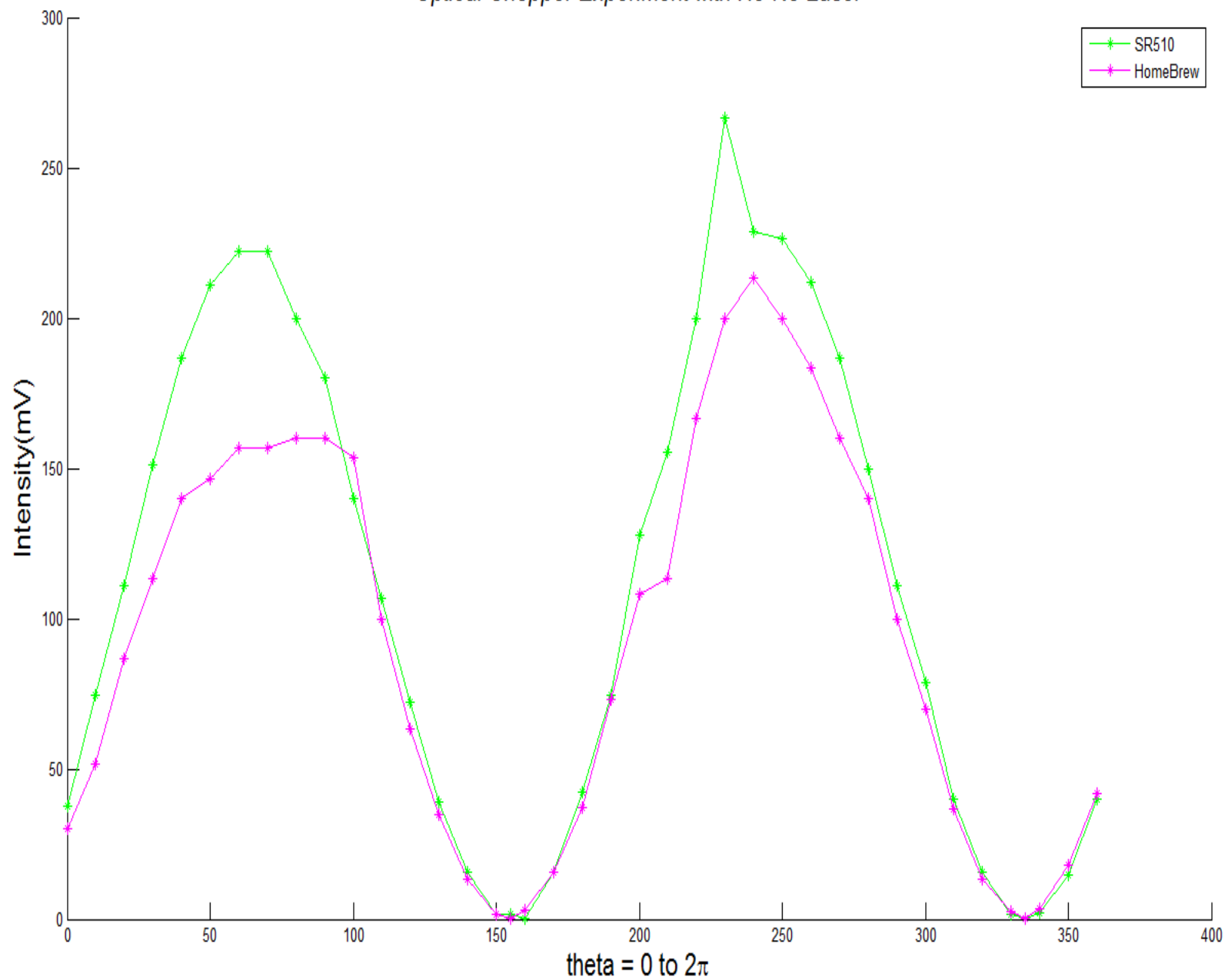
# Optical Chopper Experiment with He-Ne Laser




- Then tested with 650nm laser diode which has more stable output.
- Results are pretty good and the readings match with a maximum difference of 5mV at the peak of the curve.

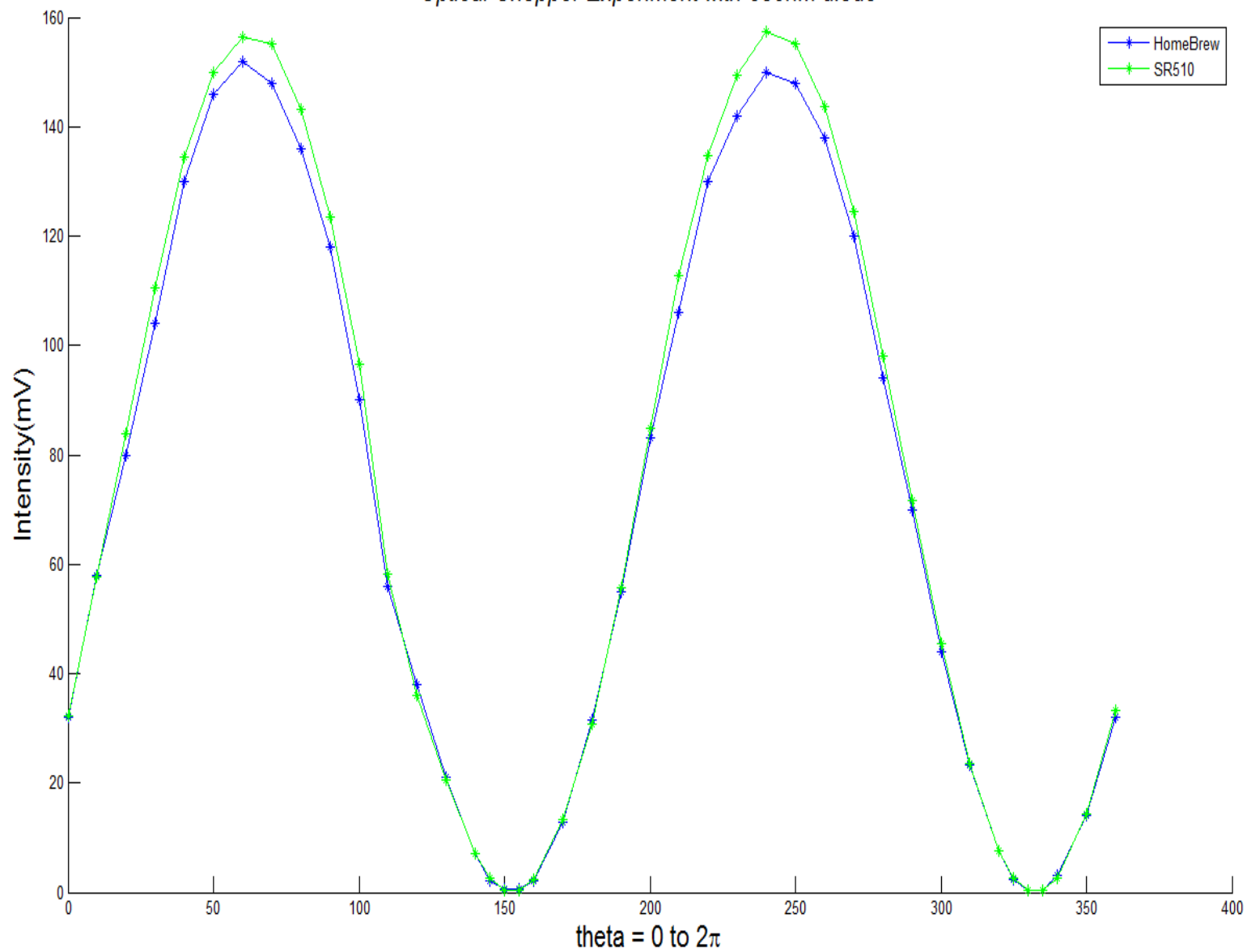*Optical Chopper Experiment with 650nm diode*



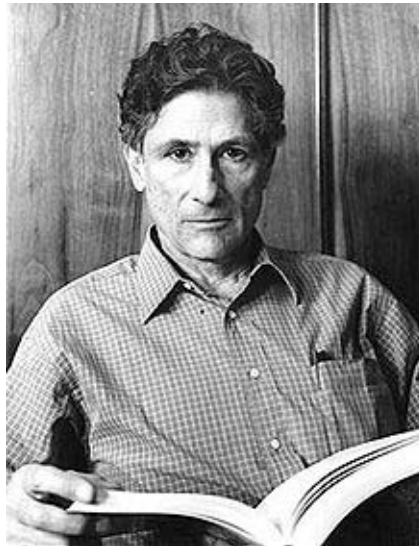- Started Afsana course: Convinced my mom I wasn't in bad company.
- Too much noisy post-colonialism and Saidian secularism. I can't hear myself!



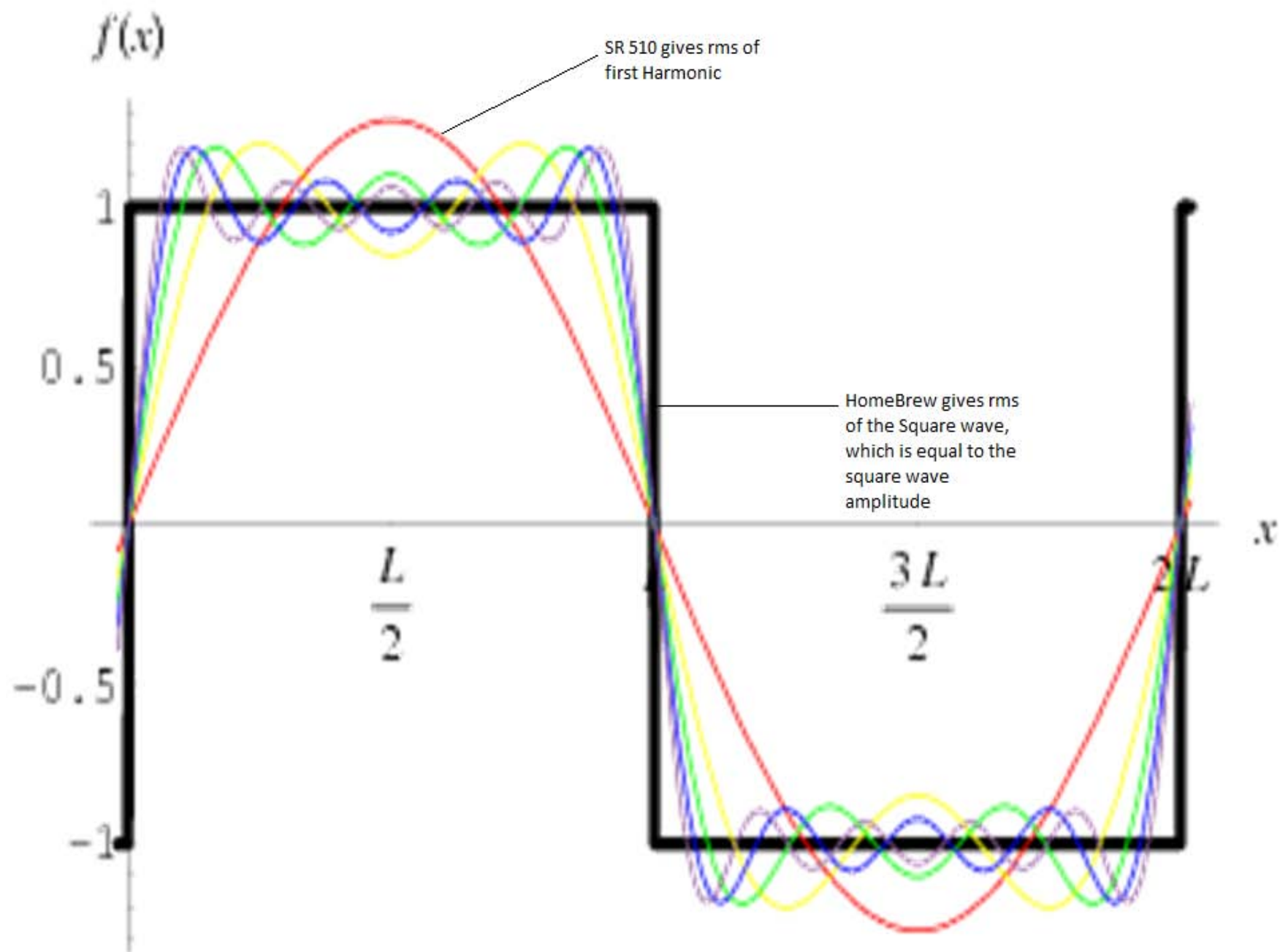
# What do the measurements mean?


- Lock-In measures rms value of that component of input signal whose frequency is equal to the reference frequency.
- If input is a square wave of 1KHz, for example, the SR510 would measure the rms value of the first harmonic of the square wave.
- This is accomplished by two sine wave multipliers.
- Walsh demodulator circuits approximate sine-wave multiplication




- The home-brew lock-in is a bit old-fashioned.
- It multiplies the input signal with a square wave.
- Thus it multiplies the input signal with all of its harmonics.
- This could generate spurious outputs if a heavy noise component resides at one of the harmonics.



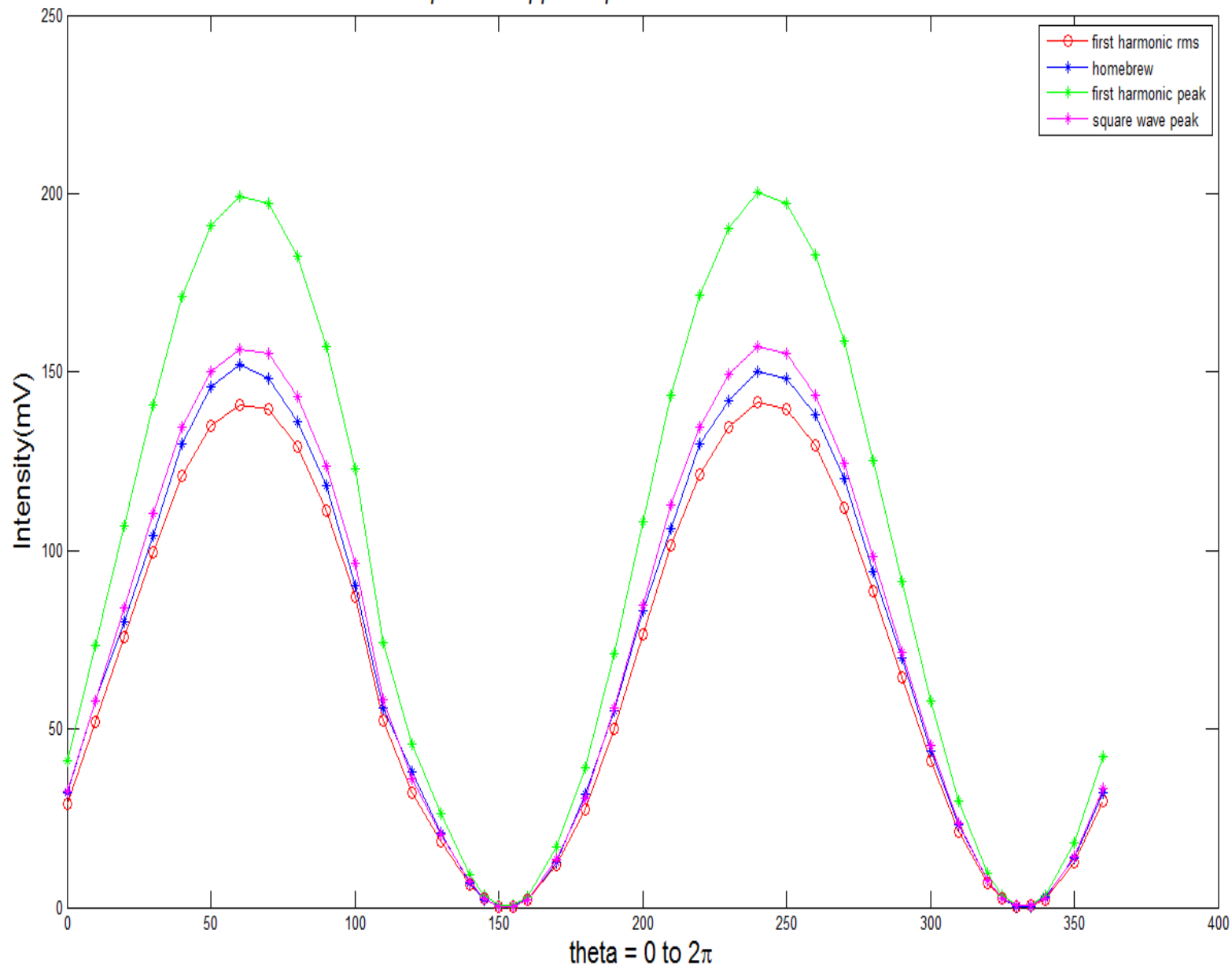*Optical Chopper Experiment with 650nm diode*




# Phase Shifter

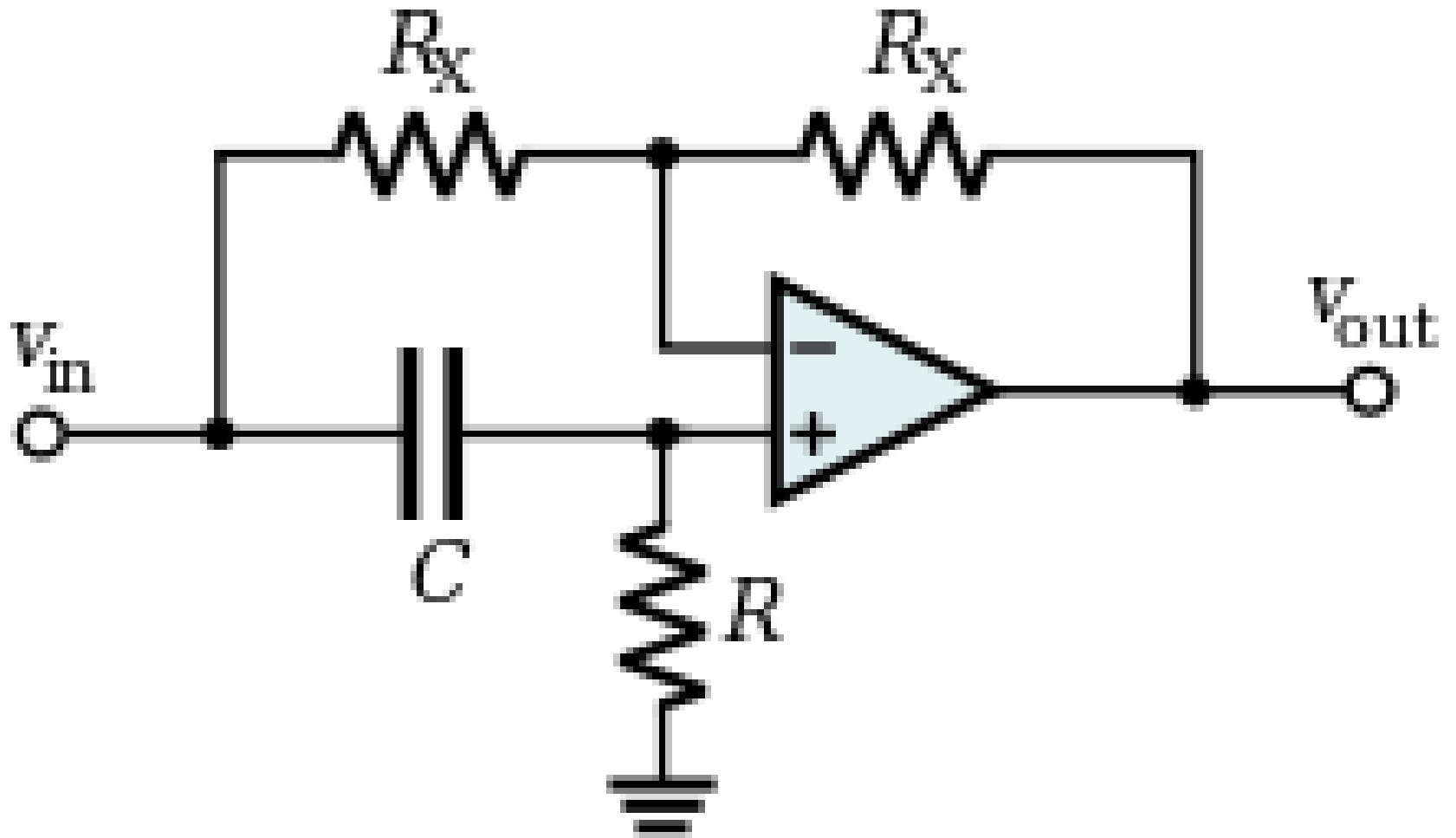

# Phase Shifter

- Unity Gain for all frequencies
- Phase shift =  $\pi - 2 \cdot \arctan(\omega RC)$  where  $\omega$  is signal frequency
- It's unlike a PLL which keeps a constant phase difference between input and output.
- Can be used in two ways:
  1. Vary the phase until DC output goes to maximum
  2. Measure the value at one particular phase, and then add a 90 degree shift and then measure the value at that phase. The root of the sum of squares of these values should be equal to maximum value measured by method 1.

# Phase Shifter Used in Homebrew Lock-in

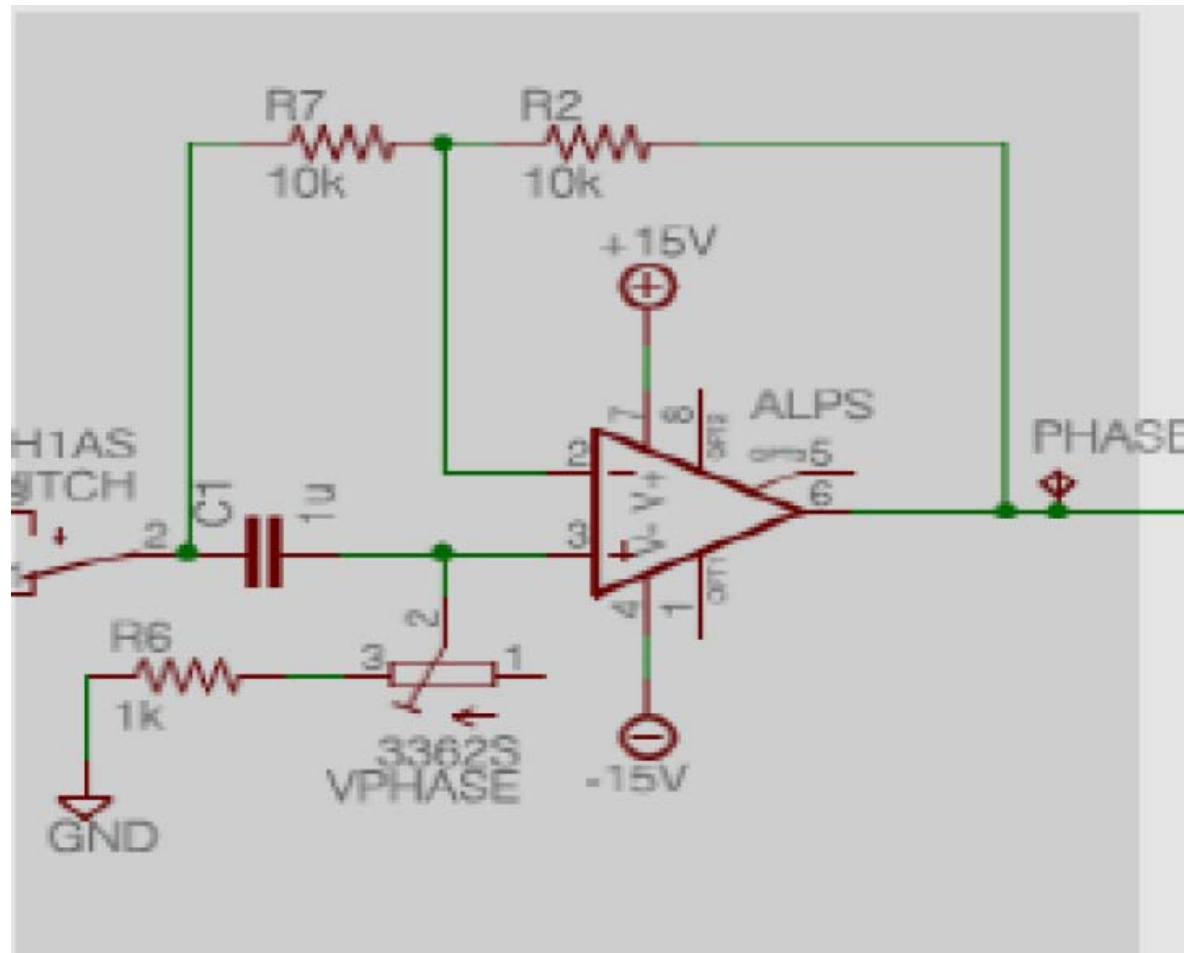

Power Supply


Input

Capacitors

High Passed Output

Rotary Switch

Variable  
Resistor

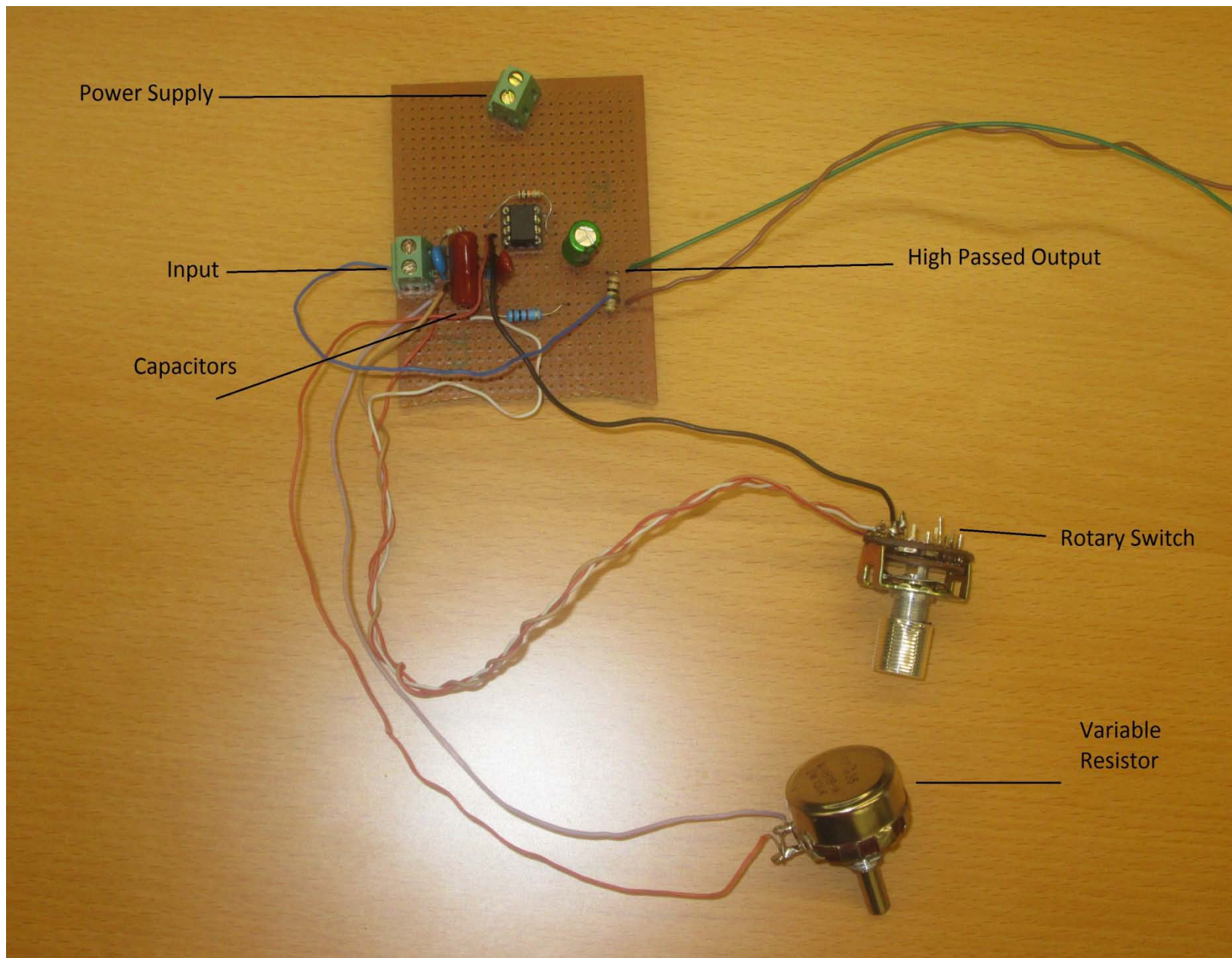



# PCB

- Tried to follow the Noise-reduction techniques in routing.
- 0.76 mm thick Al box for shielding.



# PCB Pics

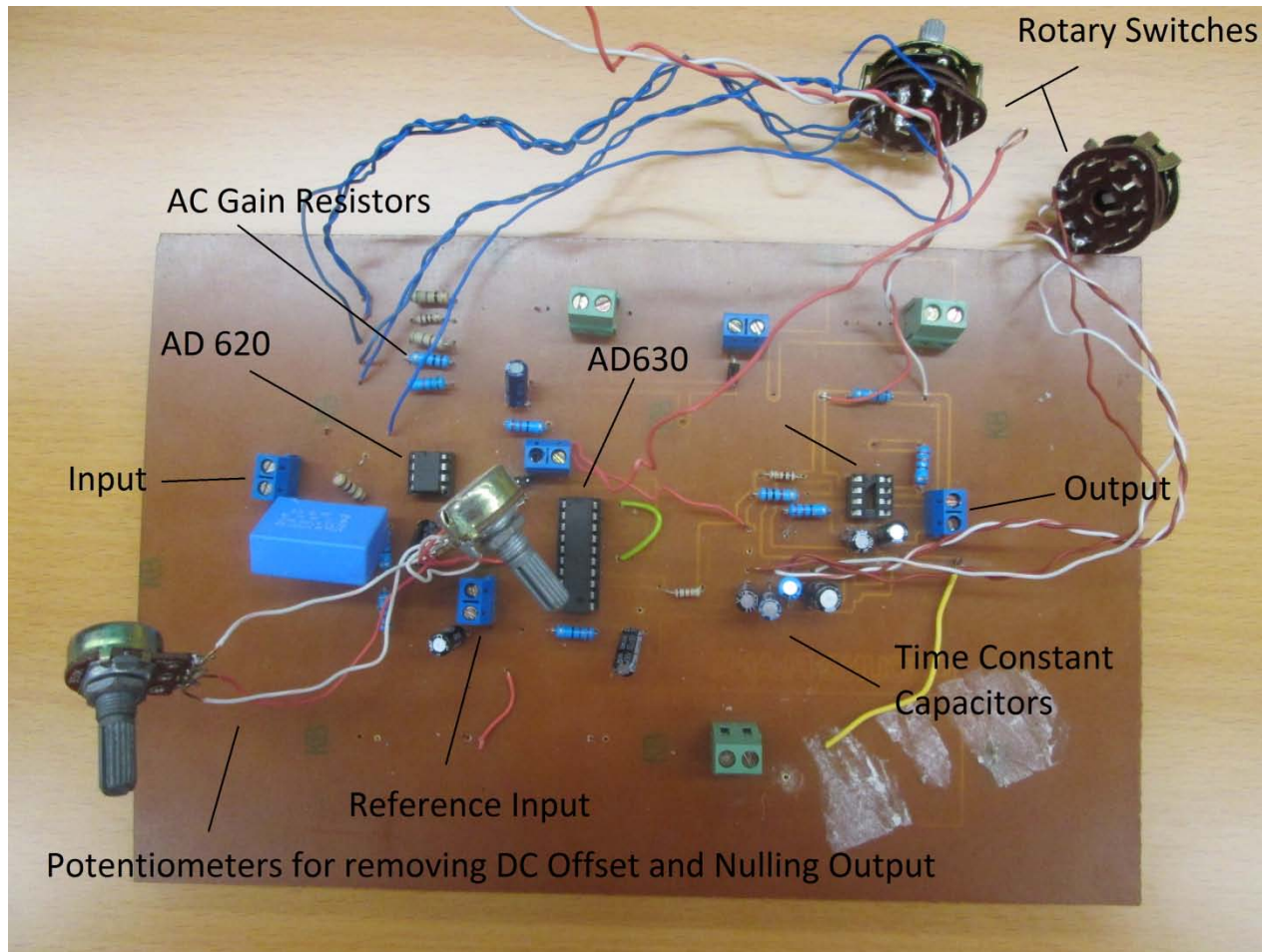


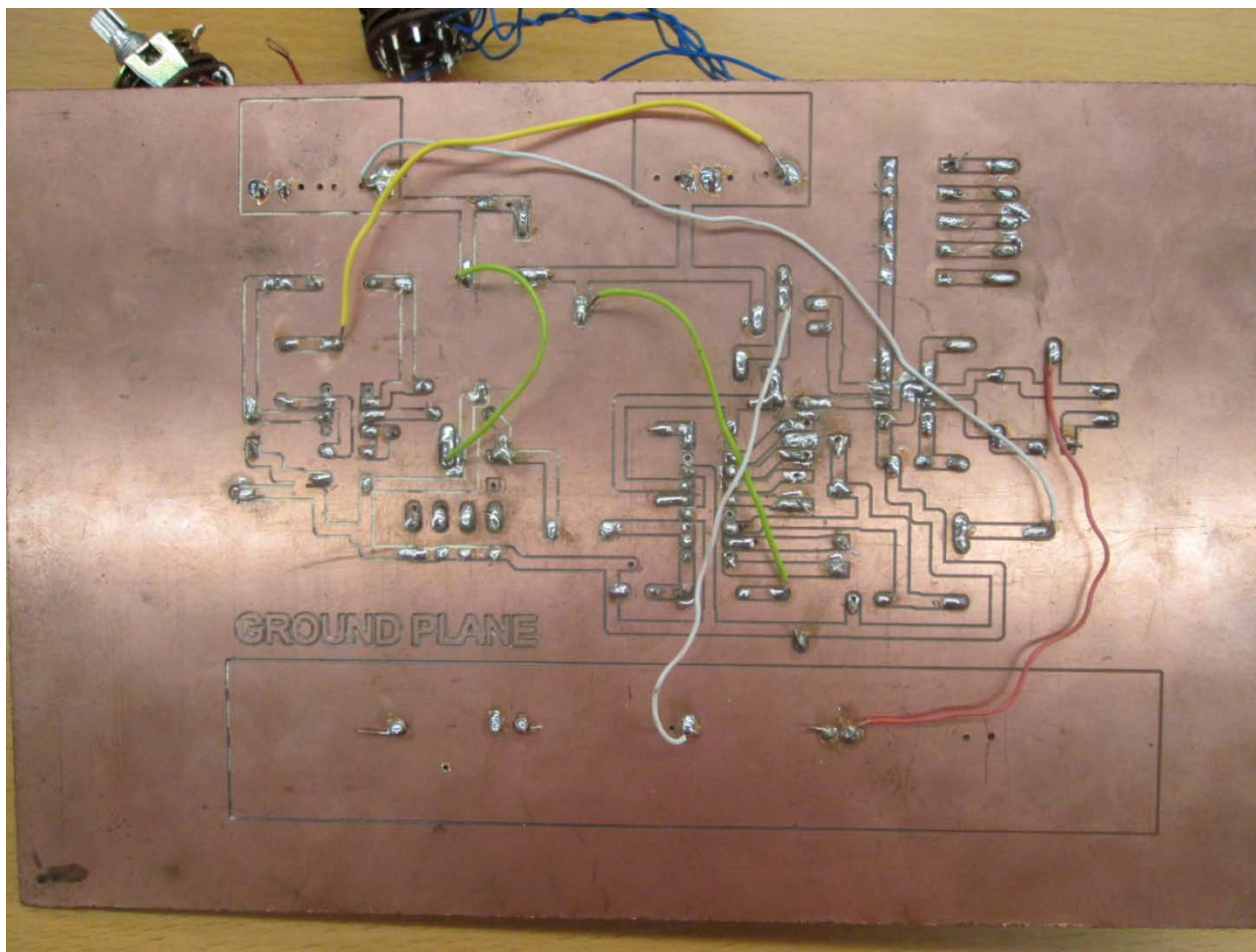








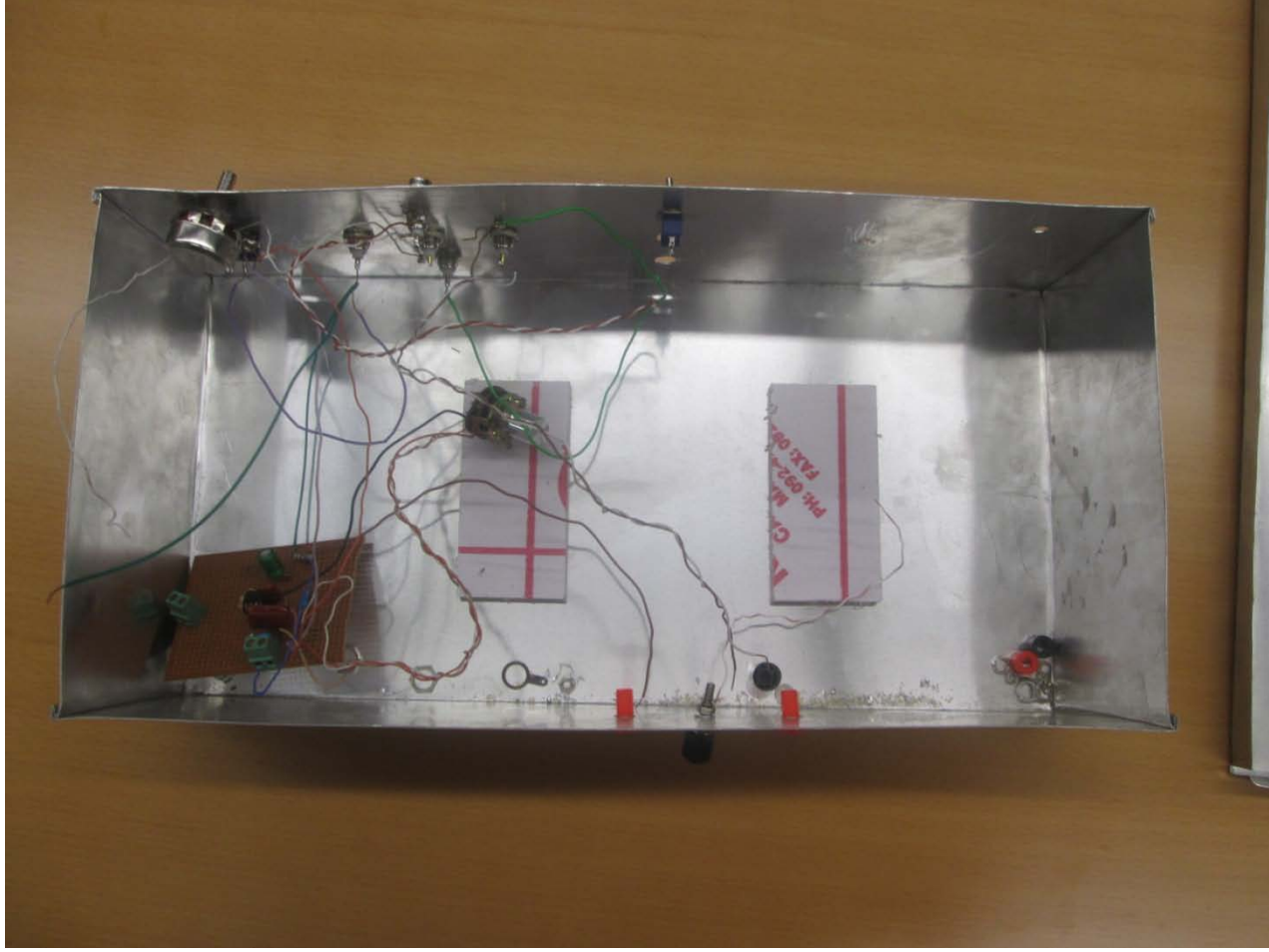


# Constant Current Source

- Maintains constant current by varying the voltage across a load, or by varying the load across which there is a constant potential drop.
- Maximum Current allowed 10mA.
- Temperature Co-efficient of  $(227/R)\mu\text{Amp}$  per degree centigrade.
- Can also be used in temperature measurement applications.

# Basic 2-Terminal Current Source

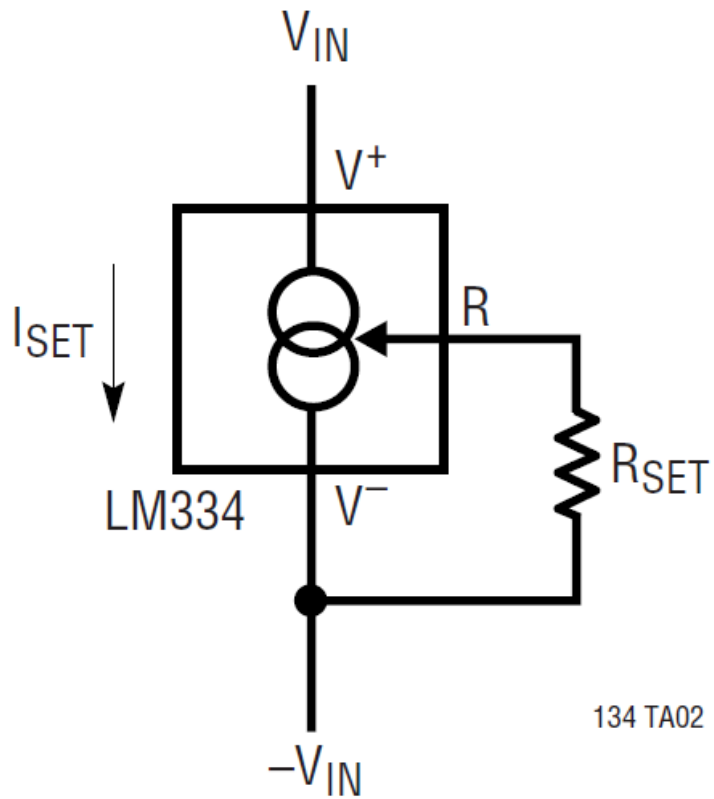
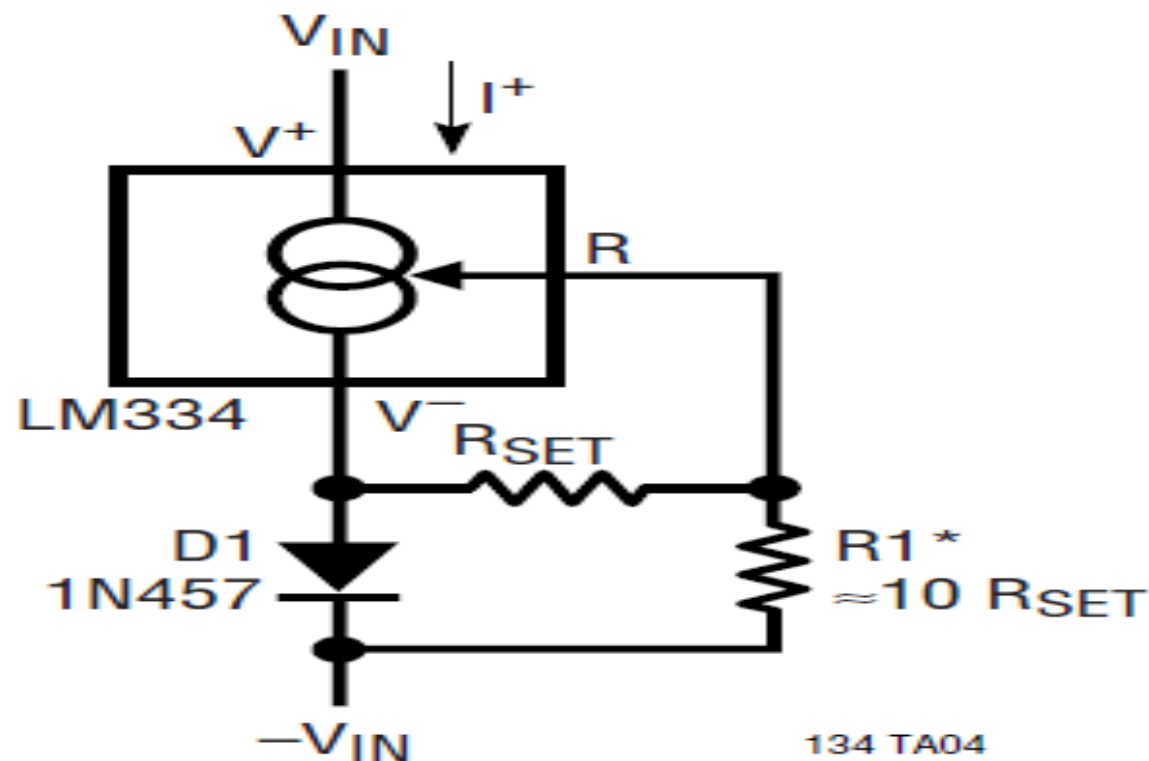
## Zero Temperature Coefficient Current Source



\*SELECT RATIO OF  $R1$  TO  $R_{SET}$  TO OBTAIN ZERO DRIFT.  $I^+ \approx 2 I_{SET}$ .



# Thank You Physlab People!

- For providing me the opportunity to **work on** such a fascinating project.
- For helping me out with the tiniest bits.
- For making my summer productive, or I'd still be playing FIFA 13.
- For providing me the opportunity to discover the clean signals beneath the noise of Lahore, its people and its rickshaws!

Muhammad yousaf  
muhammadyousaf.lums@gmail.com

